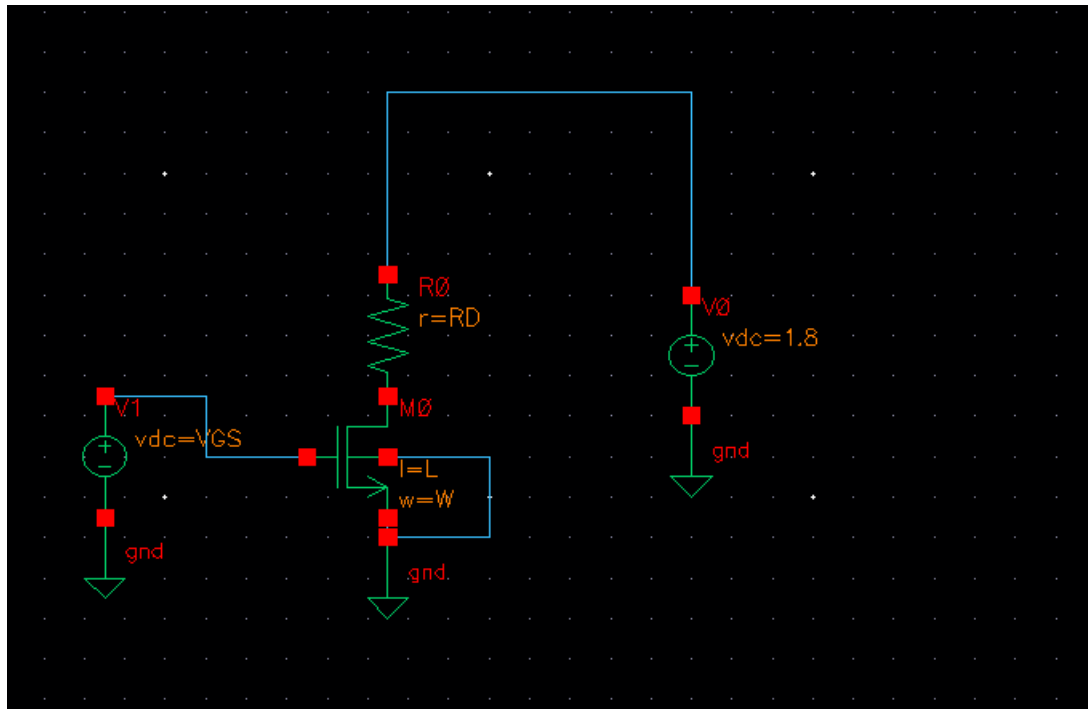


Lab 02 Common Source Amplifier

PART 1: Sizing Chart

- 1 ASSUMING CM OUTPUT = $V_{RD} = V_{DD}/2$ AND GIVEN THE DC BIAS CURRENT, DETERMINE THE VALUE OF R_D .



$$R_D = \frac{1.8 - 0.9}{150\mu} = 6K \Omega$$



$$V_{rd} = 0.9 V$$

- 2 GIVEN A_v AND V_{RD} , CALCULATE THE REQUIRED V^* (AGAIN NOTE THAT $V^* \neq V_{ov}$ FOR A REAL MOSFET). LET'S NAME THIS VALUE V_{Q^*} .


$$|A_v| = \frac{2V_{rd}}{V^*}, V^* = \frac{2V_{rd}}{|A_v|}$$

$$V^* = \frac{2 * 0.9}{6} = 0.3 V$$

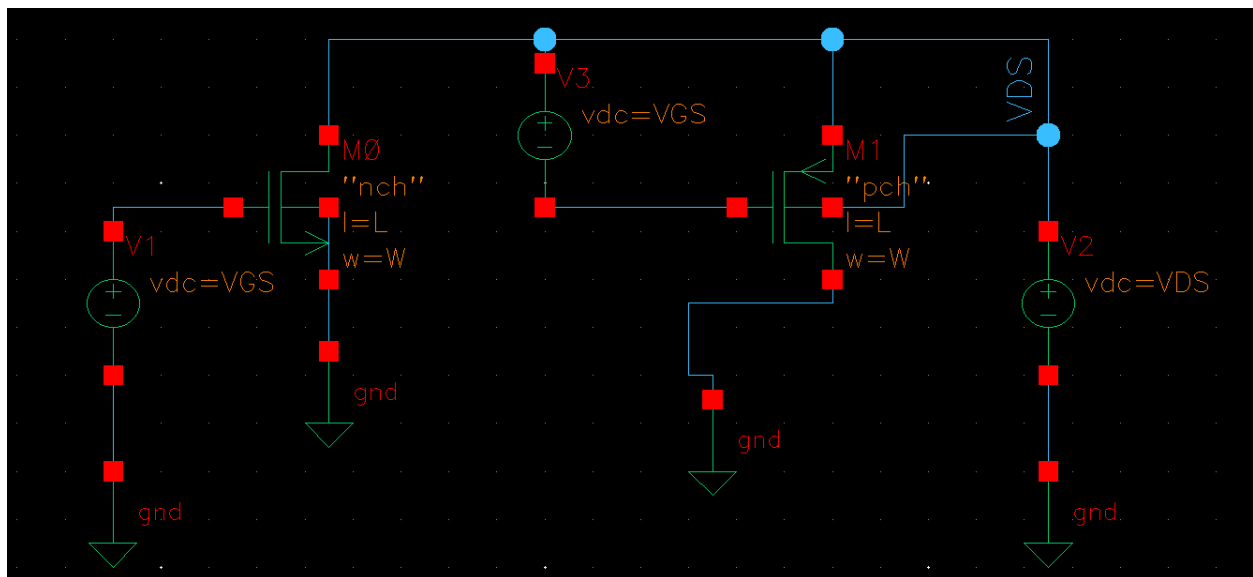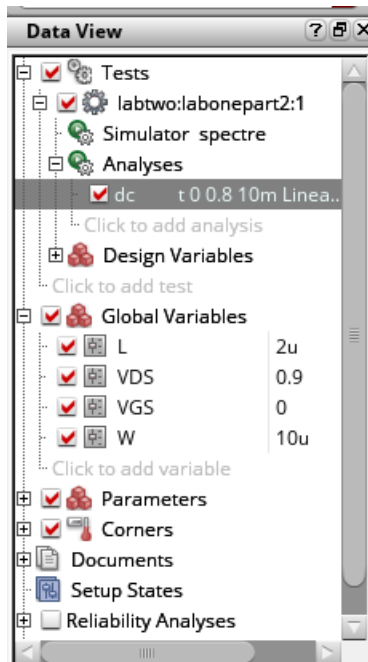3 CREATE A TESTBENCH FOR NMOS AND PMOS CHARACTERIZATION (WE WILL USE THE PMOS LATER IN PART 2 OF THIS LAB). Use $W = 10\mu m$ (WE WILL UNDERSTAND WHY SHORTLY) AND $L = 2\mu$




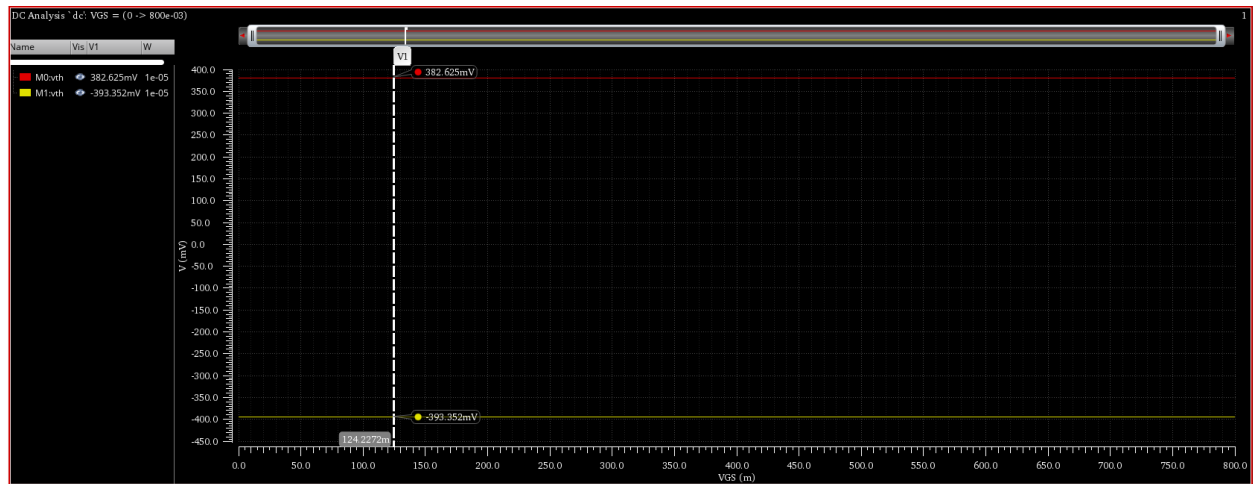4 SWEEP V_{GS} FROM 0 TO $\approx V_{TH} + 0.4V$ WITH 10mV STEP. SET $V_{DS} = V_{DD}/2$.




$|V_{th}|$ for Nmos is 382.6mv , for Pmos 393.352 .

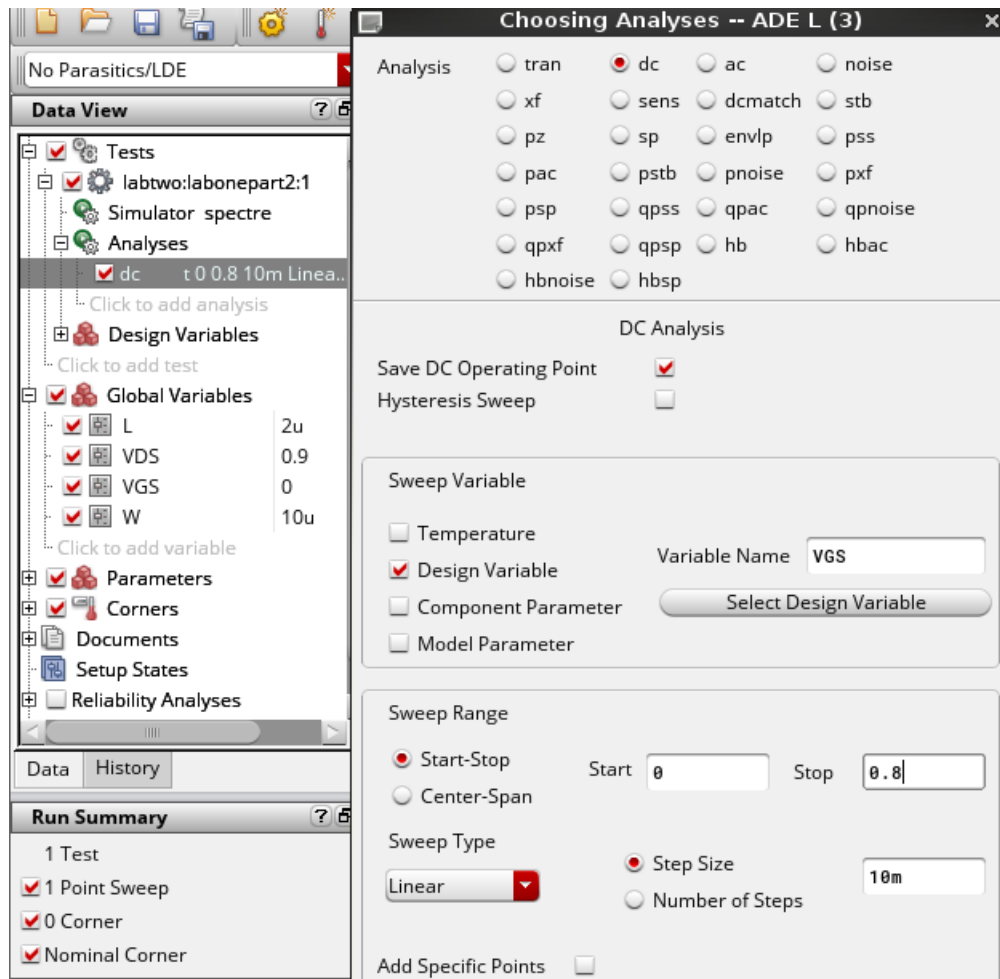We will sweep V_{GS} from 0 to $\approx 0.4 + 0.4 = 0.8v$




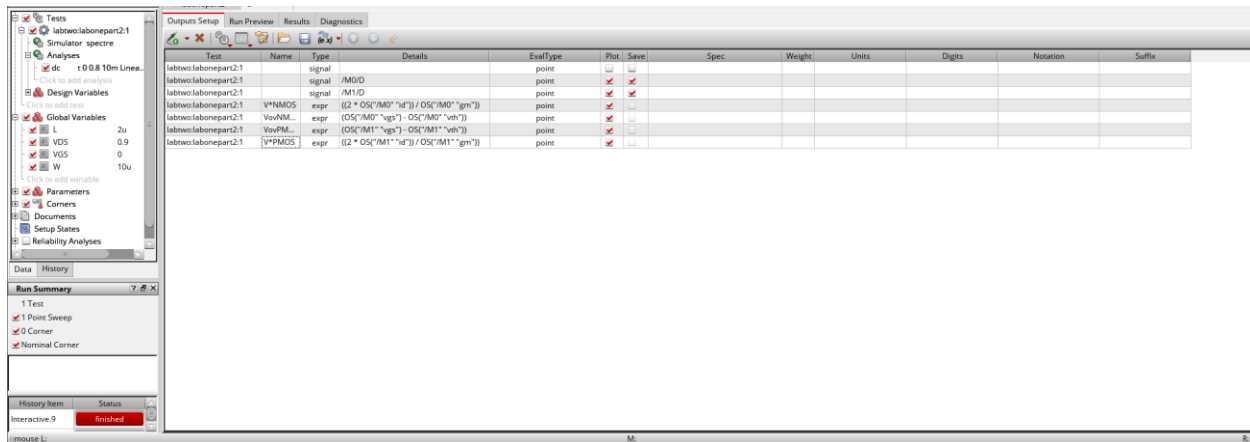- 5 COMPARE $V^* = 2ID/gm$ AND $Vov = VGS - VTH$ BY PLOTTING THEM OVERLAID. USE THE CALCULATOR TO CREATE EXPRESSIONS FOR V^* AND Vov . EXPORT THE EXPRESSIONS TO ADEXL.






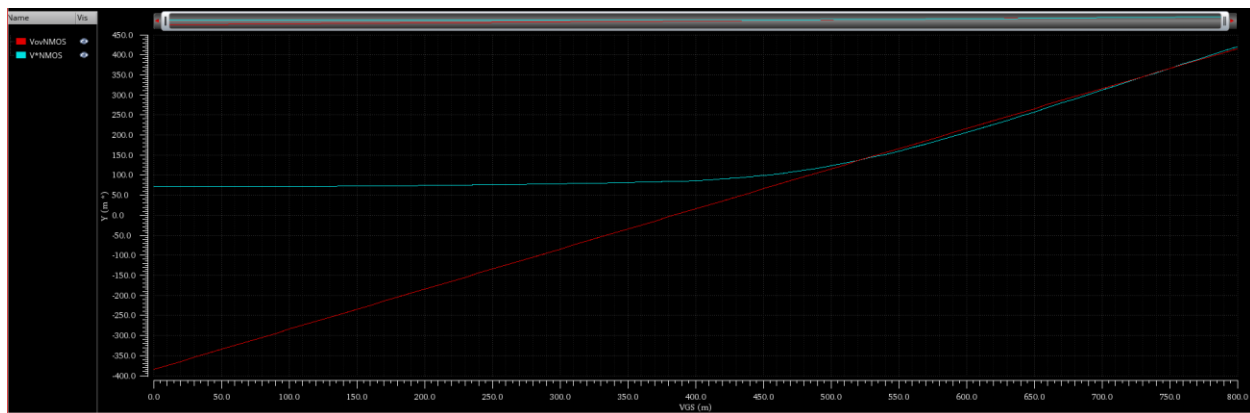6 PLOT V^* AND V_{ov} OVERLAID VS V_{GS} . MAKE SURE THE Y-AXIS OF BOTH CURVES HAS THE SAME RANGE.



NMOS

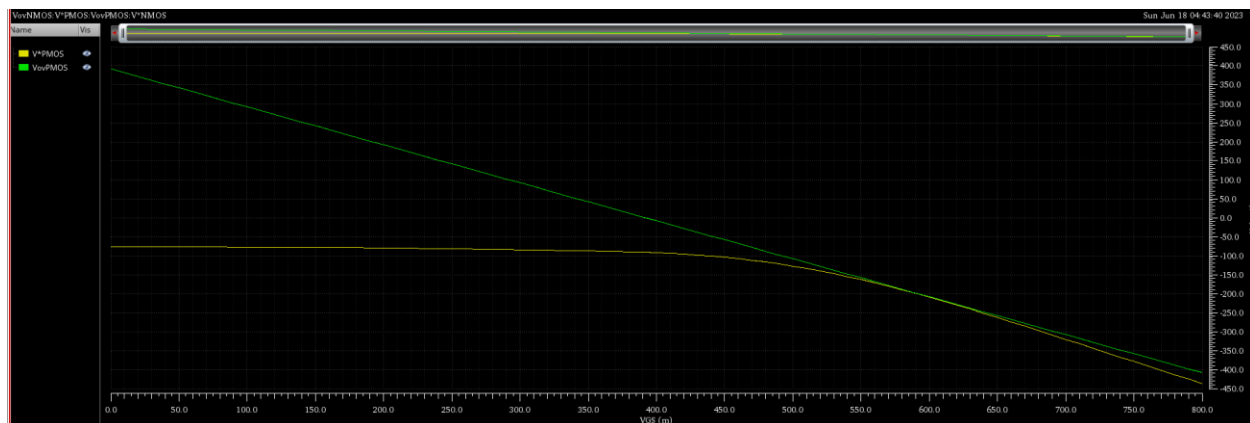


PMOS

NOTE : weak inversion (near-threshold and subthreshold operation) the behavior is quite far from the square-law , the beginning of the strong inversion region, V^* and V_{ov} are relatively close to each other

(i.e., square-law is relatively valid) , but the strong inversion (high V_{ov}) it is not shown clearly because we swept V_{gs} to only $(V_{th}+0.4)$.


7 ON THE V^* AND V_{ov} CHART LOCATE THE POINT AT WHICH $V^* = V_{Q^*}$.
FIND THE CORRESPONDING V_{ovQ} AND V_{GSQ} .

NMOS :

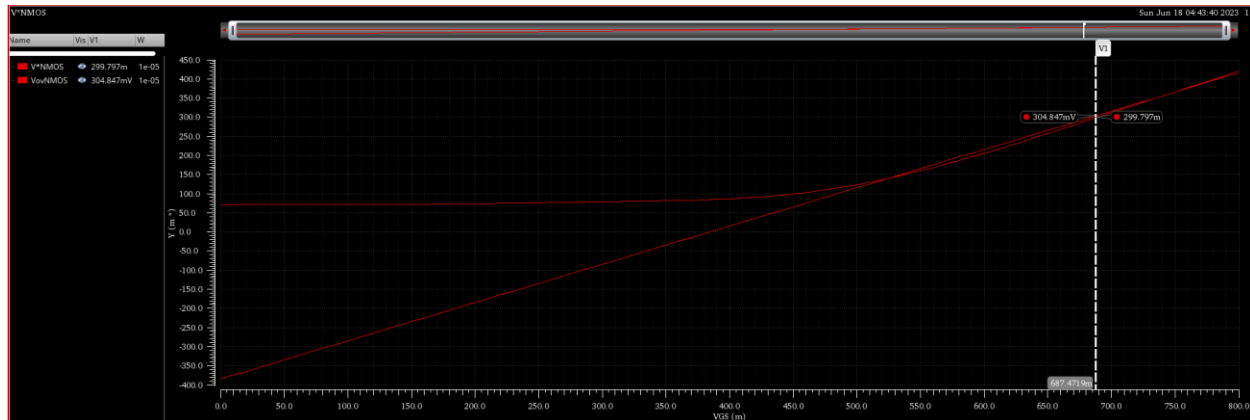

$$V_{ovq} = 304.85m \quad \&\& \quad V_{GSq} = 687.47m$$




Pmos :

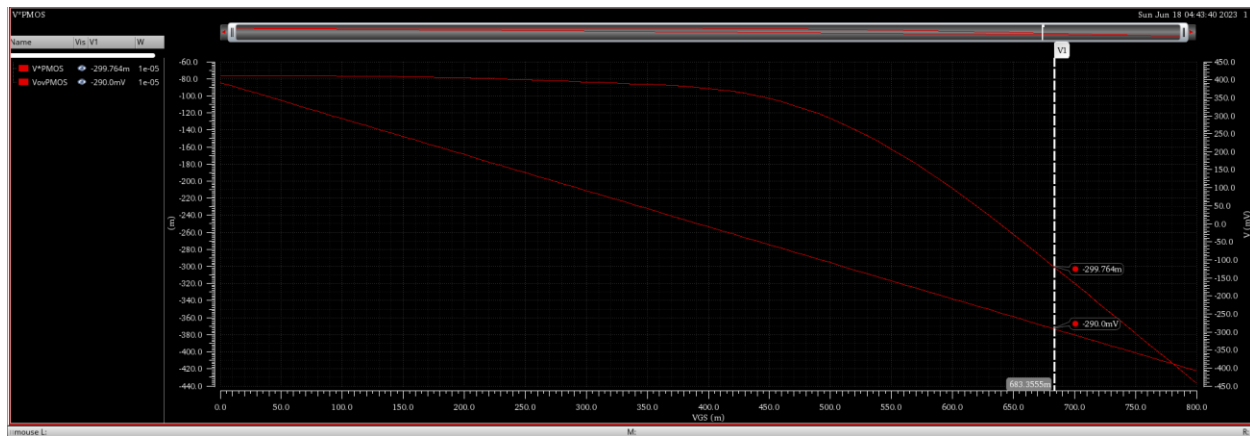


$$|V_{ovq}| = 290 m \quad \&\& \quad |V_{GSq}| = 683.35m$$

8 PLOT ID , gm , AND gds VS VGS . FIND THEIR VALUES AT $VGSQ$. LET'S NAME THESE VALUES IDX , gmX , AND $gdsX$.



NMOS:

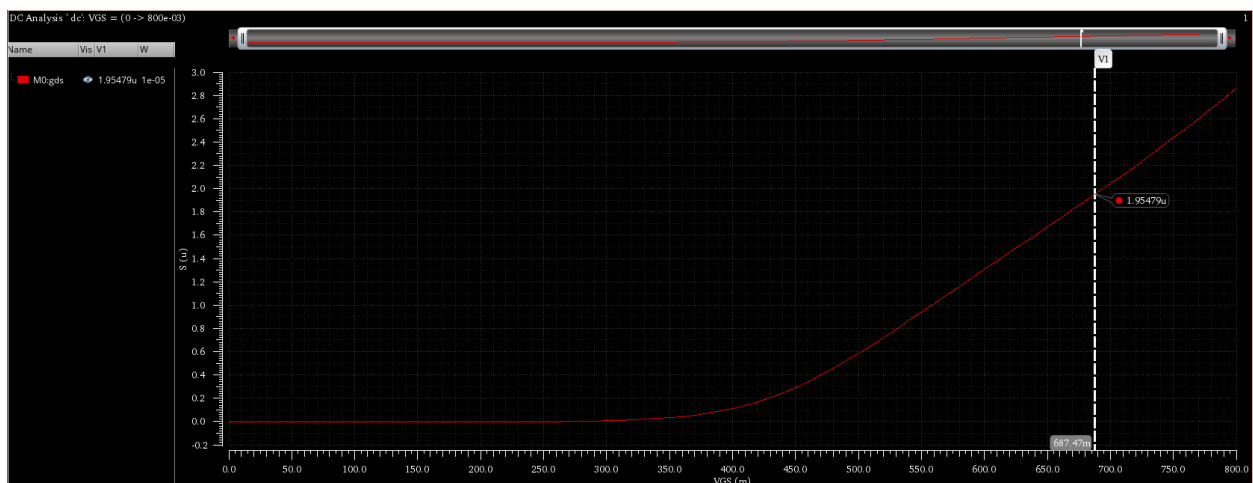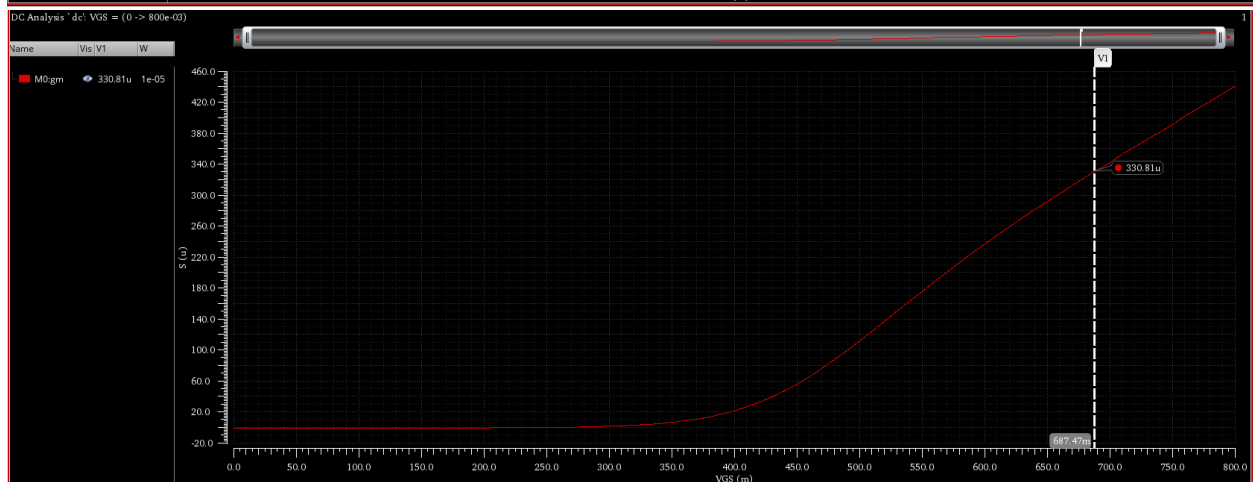
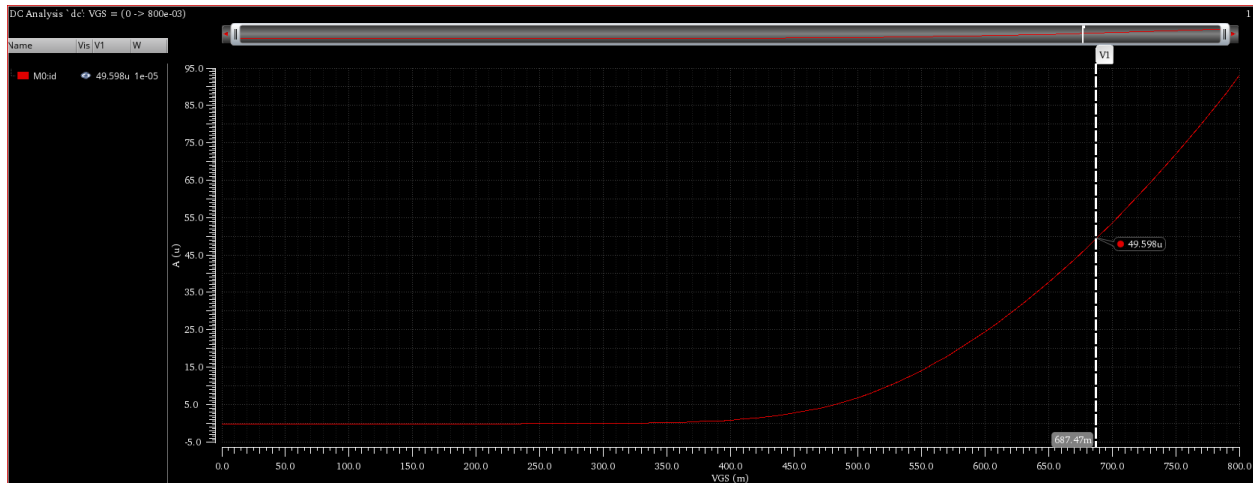


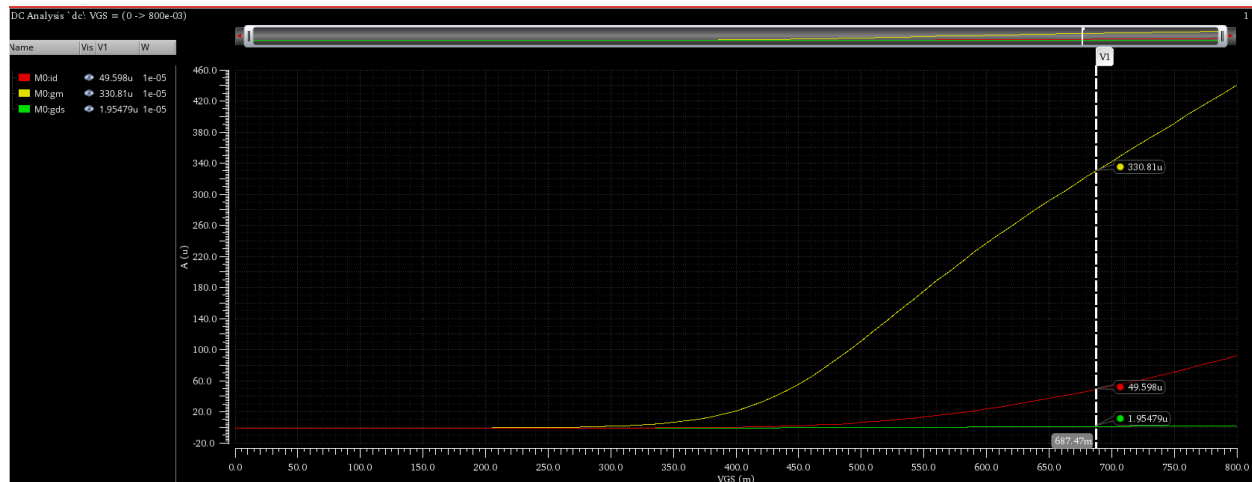

$$ID_X = 49.598 \mu A, \quad g_{mX} = 330.81 \mu, \quad g_{dsX} = 1.95479 \mu$$

PMOS:

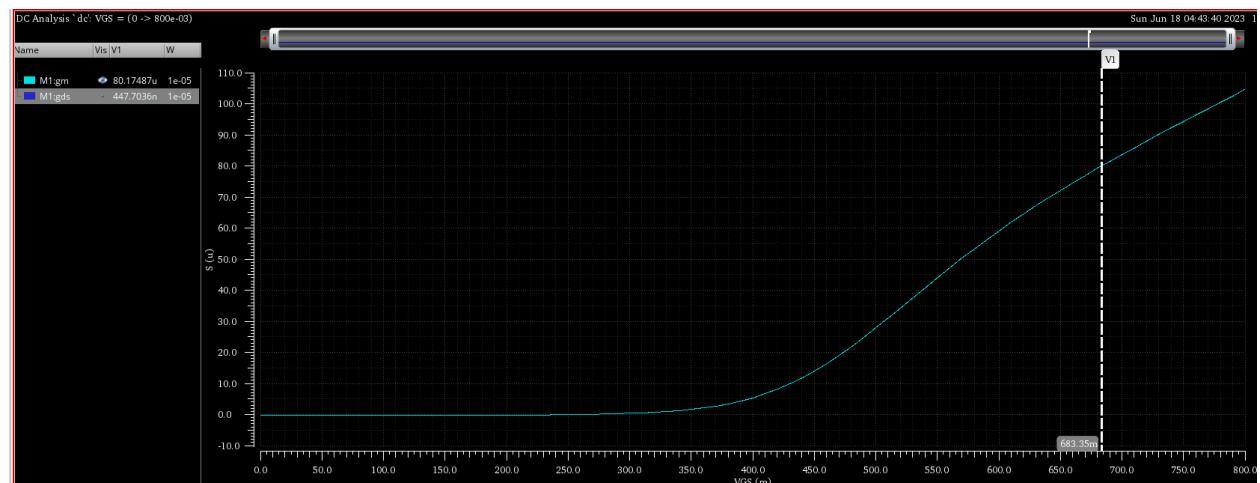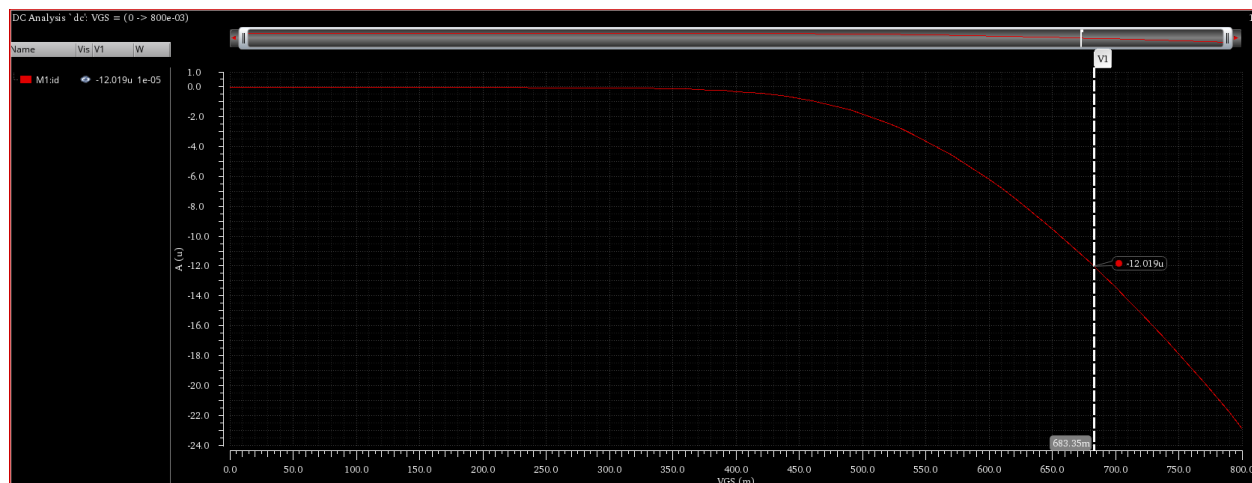

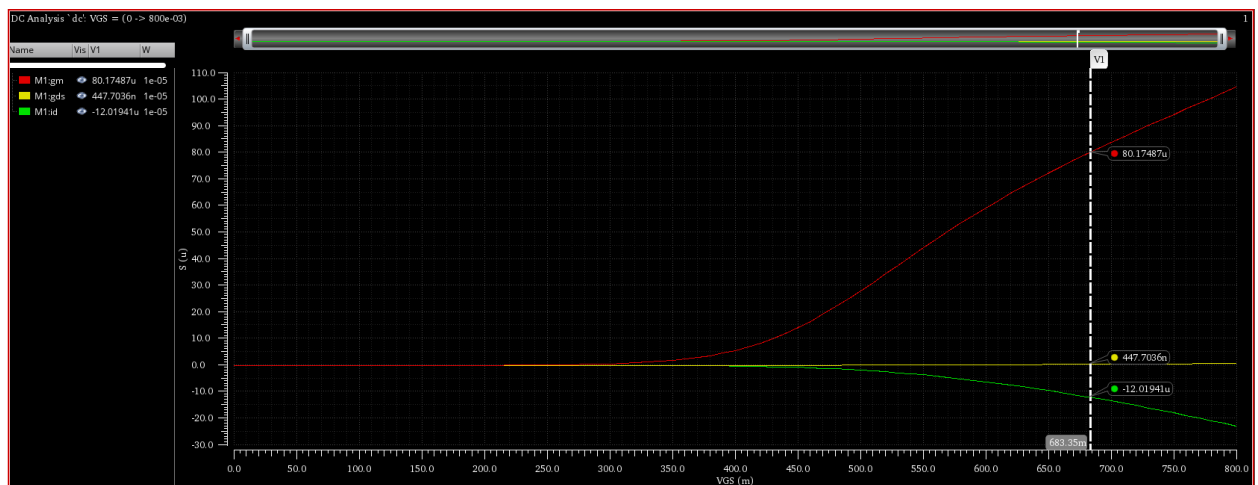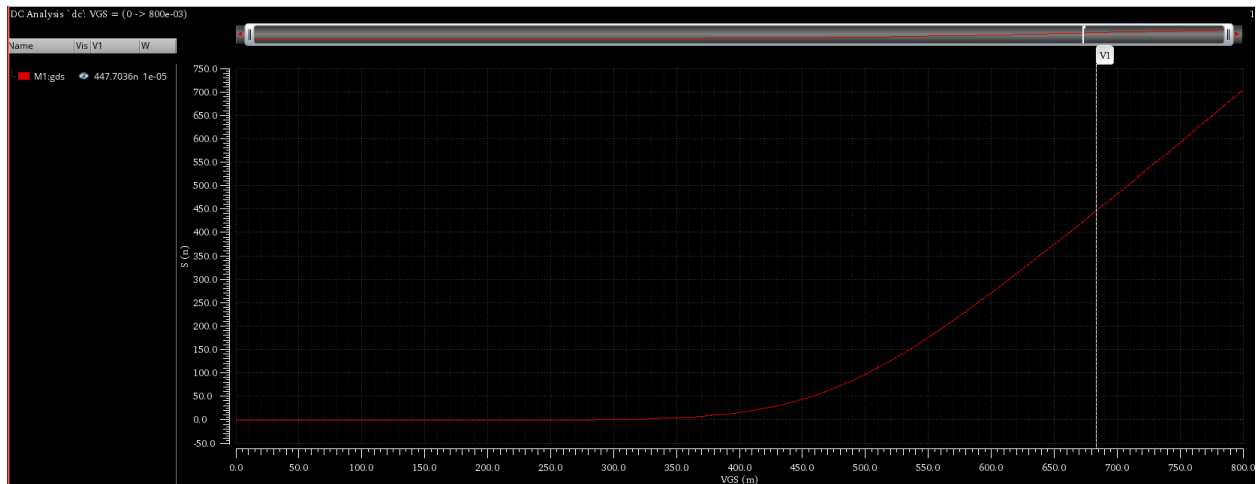

$$|ID_X| = 12.019 \text{ uA} , gm_X = 80.1745 \text{ u} , gds_X = 447.7036 \text{ n}$$

9 CALCULATE **W**

$$W_{nmos} = \frac{10\text{u} * 150\text{u}}{49.598\text{u}} = 30.243\text{u}$$

$$W_{pmos} = \frac{10\text{u} * 150\text{u}}{12.019 \text{ uA}} = 124.8\text{u}$$

• Use DC gain = -6 and ID = 150uA.

10 CALCULATE gm_Q AND gds_Q USING RATIO AND PROPORTION AND
DOUBLE CHECK THAT $Av = -gm(RD || ro)$ MEET THE REQUIRED GAIN
SPEC.

$$gm(nmos) = \frac{30.234u * 330.81u}{10u} = 1000.468u$$

$$gds(nmos) = \frac{30.234u * 1.95479u}{10u} = 5.912u$$

$$r0(nmos) = \frac{1}{gds} = 169.15K$$

$$|Av(nmos)| = 1000.468u * \frac{6k * 169.15K}{6k + 169.15K} = 5.797 \sim 5.8$$

$$gm(pmos) = \frac{124.8u * 80.1745u}{10u} = 1000.577u$$

$$gds(pmos) = \frac{124.8u * 447.7036n}{10u} = 5.587u$$



$$r0(pmos) = \frac{1}{gds} = 178.97K$$

$$|Av(pmos)| = 1000.577u * \frac{6k * 178.97K}{6k + 178.97K} = 5.8$$

The results meet the specs.

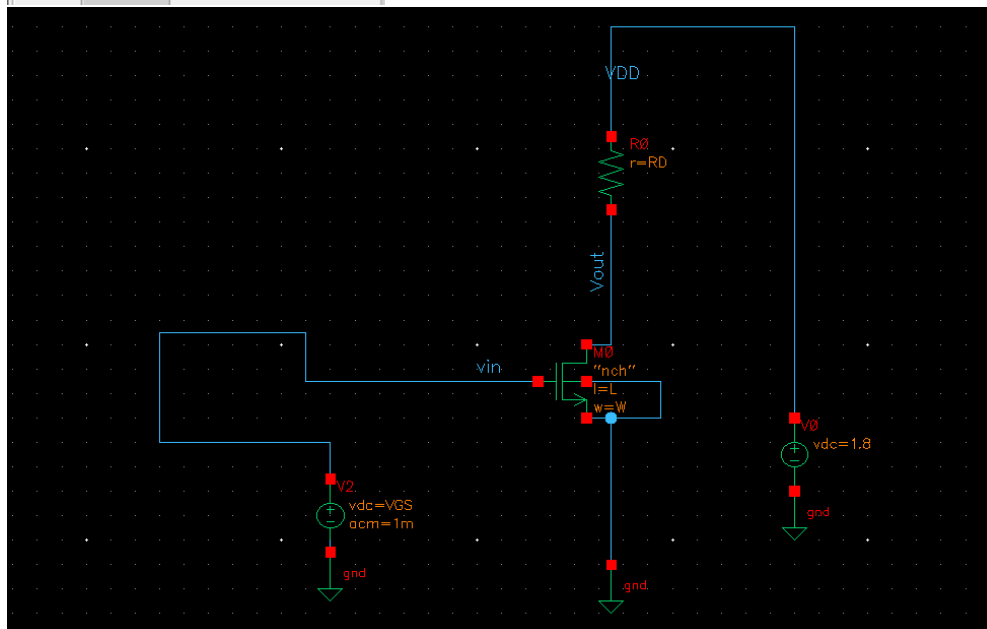
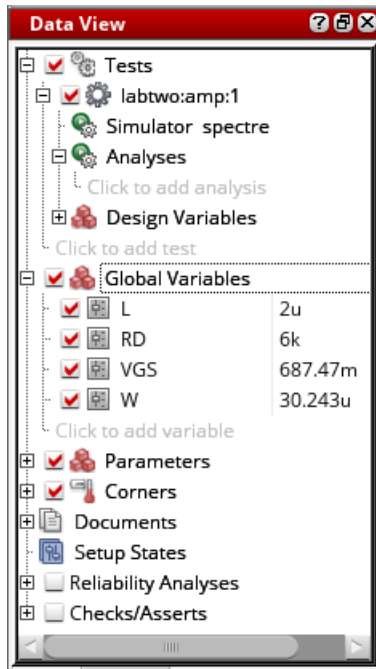
PART 2: CS Amplifier

- 1 CREATE A TESTBENCH FOR THE RESISTIVE LOADED CS AMPLIFIER USING THE V_{GSQ} , R_D , L , AND W THAT YOU GOT FROM THE PREVIOUS PART



Assume ac small signal 1 m to find the gain in required 6 .

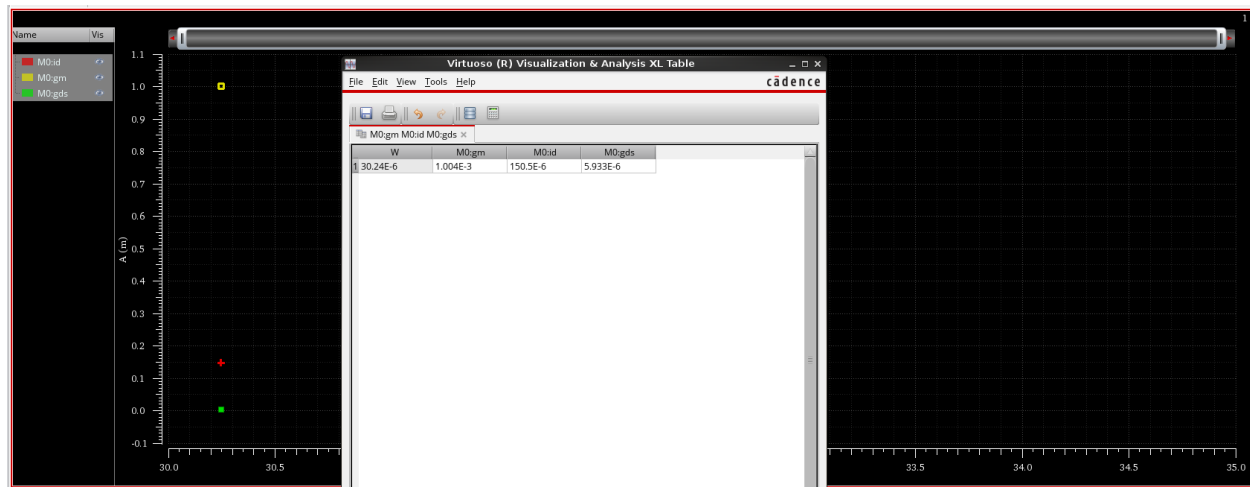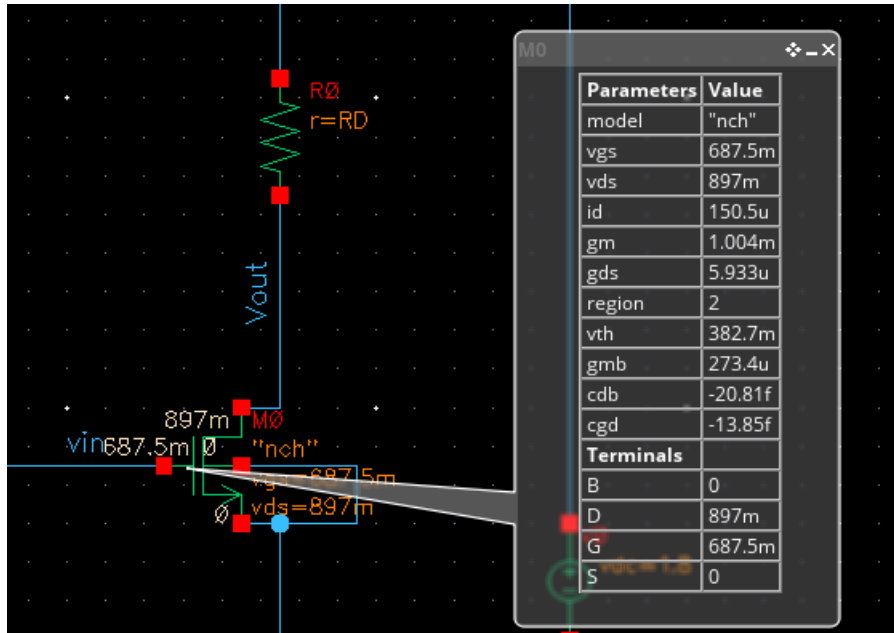- 2 SIMULATE THE DC OP. REPORT A SNAPSHOT FOR THE KEY OPERATING POINT (OP) PARAMETERS. COMPARE THE RESULTS WITH THE RESULTS YOU OBTAINED IN PART 1. SINCE WE USED CHART-BASED DESIGN, THE RESULTS SHOULD AGREE WELL



	gm	ID	gds
Part 2	1.004m	150.5u	5.933u
Part 1	1000.468u	150u	5.912u

the results agree well.

Region is 2 which means it works in saturation.


- 3 COMPARE r_o AND R_D . IS THE ASSUMPTION OF IGNORING r_o JUSTIFIED IN THIS CASE? DO YOU EXPECT THE ERROR TO REMAIN THE SAME IF WE USE MIN L ?

$r_o = 1/g_{ds} = 168.55K$, $R_D = 6K$, $r_o \gg R_D$, $R_{eq} = \frac{6 \cdot 168.55}{6 + 168.55} k = 5.8k$, error = $\frac{6 - 5.8}{6} = 3.33\%$, yes the error is so small so it is justified to ignore r_o .

the error expected to be larger because of short channel effects (channel length modulation) as early voltage (V_A) will decrease so r_o would be smaller .

- 4 CALCULATE THE INTRINSIC GAIN OF THE TRANSISTOR.

$$|A_v| = g_m \cdot r_o = g_m / g_{ds} = 169.2$$

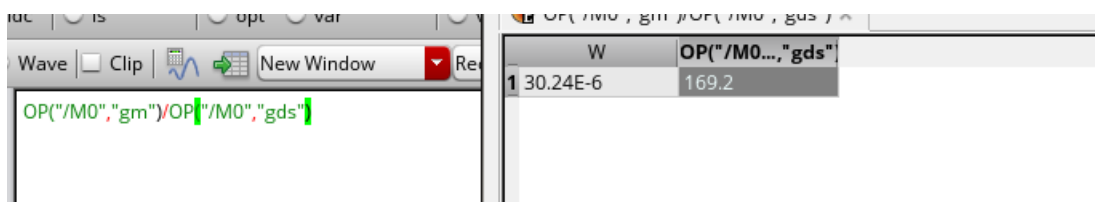

- 5 CALCULATE THE AMPLIFIER GAIN ANALYTICALLY. WHAT IS THE RELATION ($\ll, <, =, >, \gg$) BETWEEN THE AMPLIFIER GAIN AND THE INTRINSIC GAIN?

$$G_M = -g_m \text{ , } R_S = 0, v_{gs} = 0 \text{ \&\& } R_{out} = R_D || r_o$$

$$|A_v| = g_m \cdot R_D || r_o = 1.004 \cdot 10^{-3} \cdot \frac{6 \cdot 10^3 \cdot 168.55 \cdot 10^3}{6 \cdot 10^3 + 168.55 \cdot 10^3} = 5.817$$

the amplifier gain \ll the intrinsic gain , because R_d is much less than r_o so it dominates .

6 CREATE A NEW SIMULATION CONFIGURATION AND RUN AC ANALYSIS (FROM 1HZ TO 1GHZ). REPORT THE GAIN VS FREQUENCY. ANNOTATE THE DC GAIN AND MAKE SURE IT MEETS THE SPEC .

Choosing Analyses -- ADE L (2)

Analysis

☐ tran ☐ dc ☒ ac ☐ noise

☐ xf ☐ sens ☐ dcmatch ☐ stb

☐ pz ☐ sp ☐ envlp ☐ pss

☐ pac ☐ pstb ☐ pnoise ☐ pxf

☐ psp ☐ qpss ☐ qpac ☐ qpnoise

☐ qpxf ☐ qpzp ☐ hb ☐ hbac

☐ hbnoise ☐ hbzp

AC Analysis

Sweep Variable

☒ Frequency

☐ Design Variable

☐ Temperature

☐ Component Parameter

☐ Model Parameter

☐ None

Sweep Range

☒ Start-Stop Start 1 Stop 1G

☐ Center-Span

Sweep Type

Automatic

Add Specific Points ☐

Specialized Analyses


None

Enabled ☒

Options...

OK Cancel Defaults Apply Help

	expr	$\left(\frac{VF("Vout")}{VF("vin")} \right)$
	expr	$\text{phase}\left(\frac{VF("Vout")}{VF("vin")} \right)$

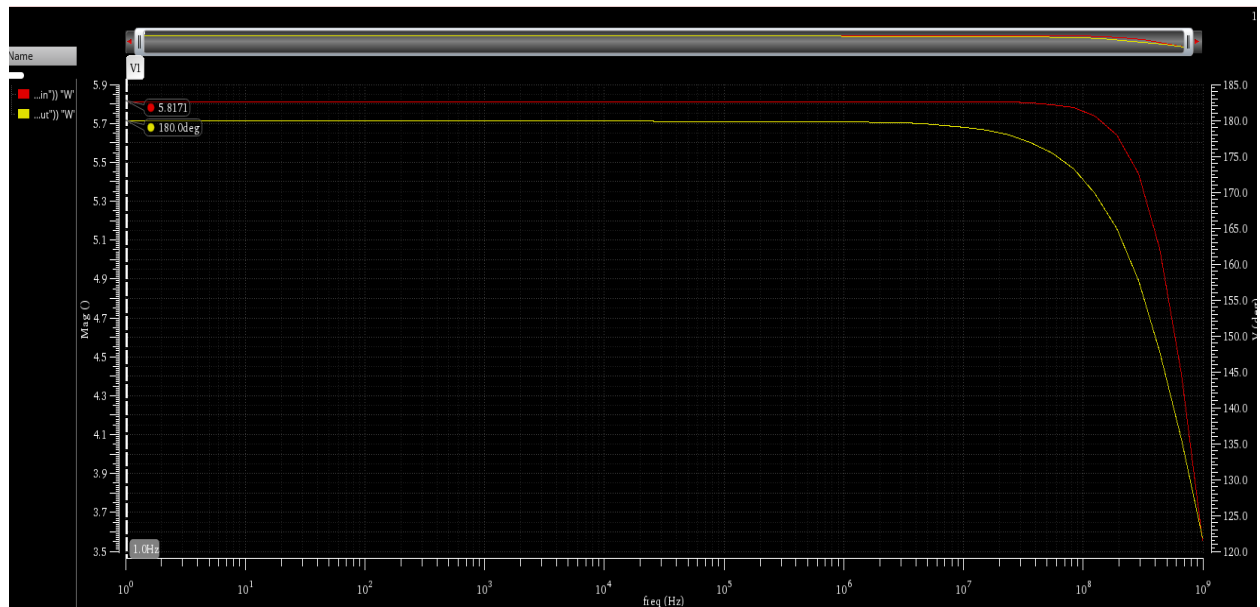

DC gain (when frequency is 1hz) is 5.8171 and also there is a 180-degree phase shift, which meets the specs, we note that when the frequency is too high (more than 10^7) the gain drops.

Gain Non-Linearity

- 1 CREATE A NEW SIMULATION CONFIGURATION. PERFORM A DC SWEEP FOR THE INPUT VOLTAGE FROM 0 TO V_{DD} WITH 2mV STEP.

Choosing Analyses -- ADE L (4)

Analysis: ☐ tran ☒ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☐ pz ☐ sp ☐ envlp ☐ pss
☐ pac ☐ pstb ☐ pnoise ☐ pxf
☐ psp ☐ qpss ☐ qpac ☐ qpnoise
☐ qpxf ☐ qpss ☐ hb ☐ hbac
☐ hbnoise ☐ hbss

DC Analysis

Save DC Operating Point ☒
Hysteresis Sweep ☐

Sweep Variable

☐ Temperature
☒ Design Variable Variable Name:
☐ Component Parameter
☐ Model Parameter

Sweep Range

☒ Start-Stop Start: Stop:
☐ Center-Span


Sweep Type

☒ Step Size
☐ Number of Steps

Add Specific Points ☐



Enabled ☒

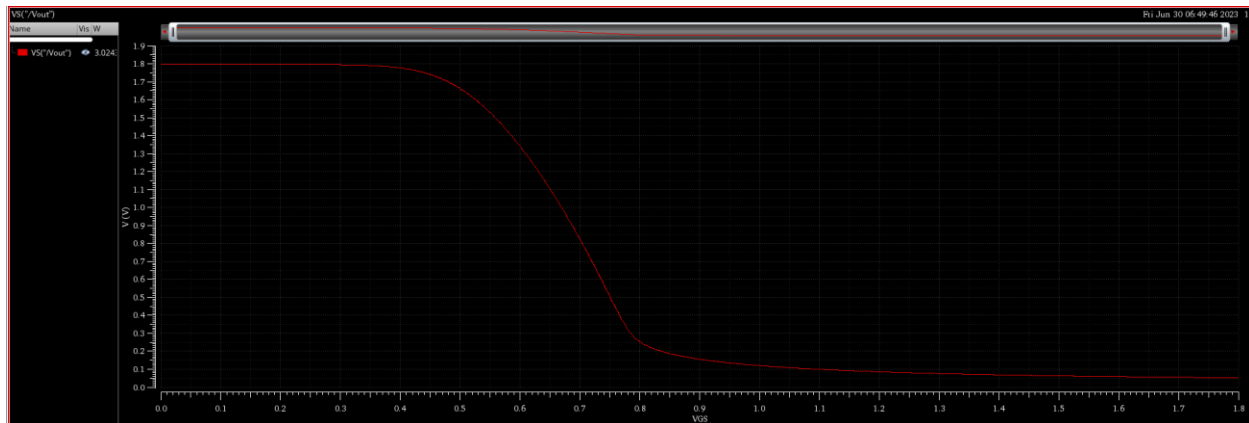2 REPORT V_{OUT} VS V_{IN} . IS THE RELATION LINEAR? WHY?



The relation is not linear, because V_{OUT} depends on I_D ($V_{OUT} = V_{DD} - I_D * R_D$), and I_D depends on $V_{GS}(\text{input})$ which approximately has quadratic relation with $V_{GS}(\text{input})$ in saturation, and actually V_{out} variation depends on V_{in} variation with the slope of this plot which is the gain which is a function of $V_{GS}(\text{input})$, and gain is not linear as it is a function of g_m, r_0 which are by the way functions of V_{in} .

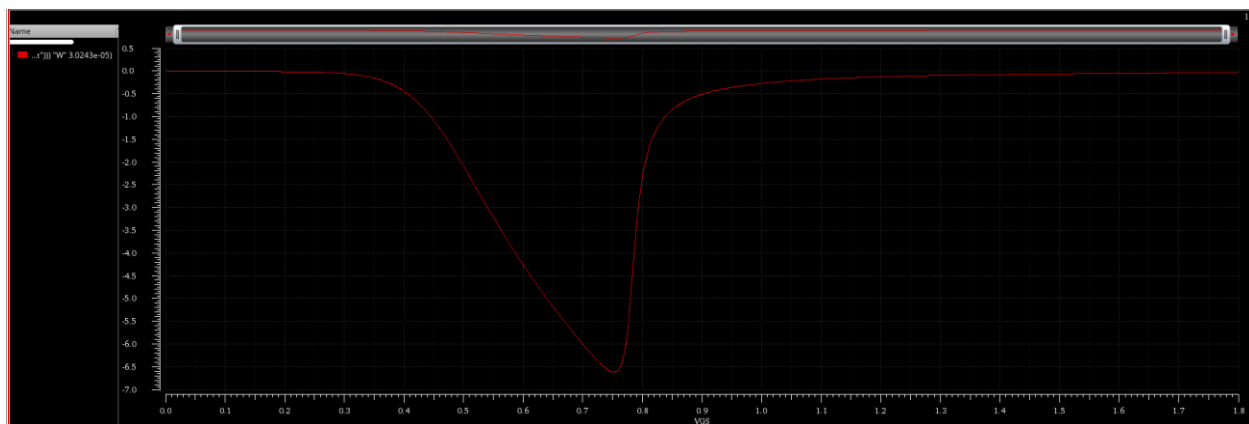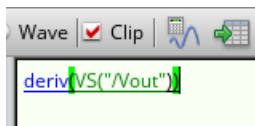
3 CALCULATE THE DERIVATIVE OF V_{OUT} USING CALCULATOR. PLOT THE DERIVATIVE VS V_{IN} . THE DERIVATIVE IS ITSELF THE SMALL SIGNAL GAIN. IS THE GAIN LINEAR (INDEPENDENT OF THE INPUT)? WHY?





No, gain is not linear because it is a function of g_m, r_0 ($|A_v| = g_m(R_D || r_0)$) which are actually functions of $V_{GS}(V_{in})$ (in case of r_0 changing V_{in} changes I_D with it, r_0

is the slope of i_d vs $V_{out}(V_{ds})$, so r_o also depends on the change of V_{in} then the gain depends on V_{in} (the input) which make it non linear.


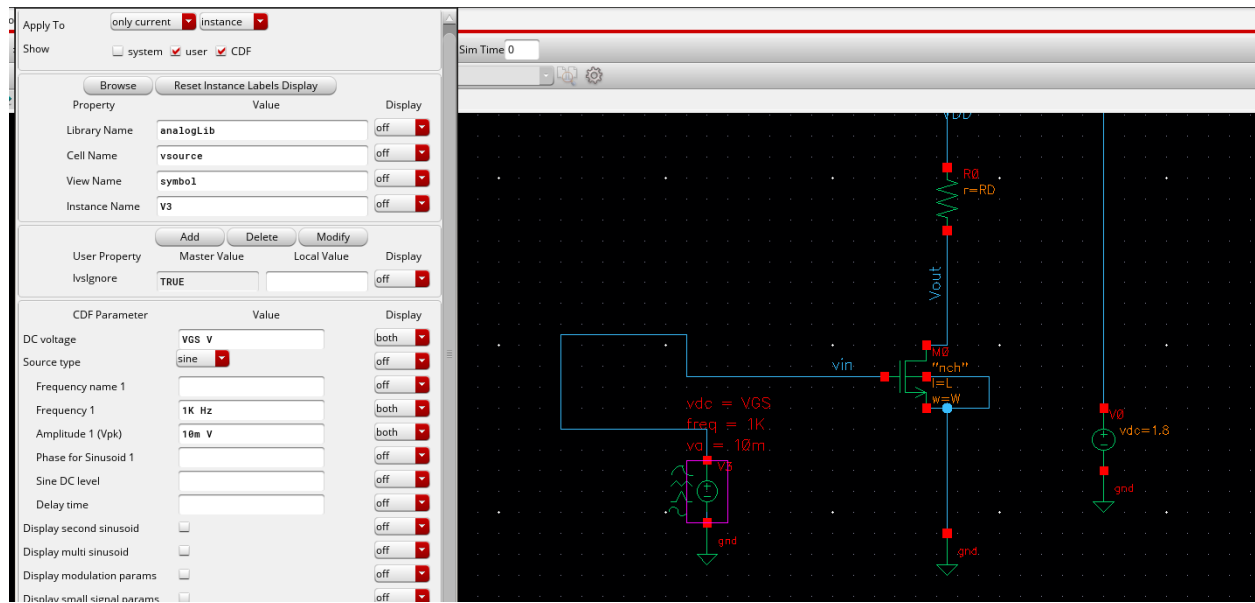
4 SET THE PROPERTIES OF THE VOLTAGE SOURCE TO APPLY A TRANSIENT STIMULUS (SINE WAVE OF 1KHZ FREQUENCY AND 10mV AMPLITUDE SUPERIMPOSED ON THE DC INPUT VOLTAGE).



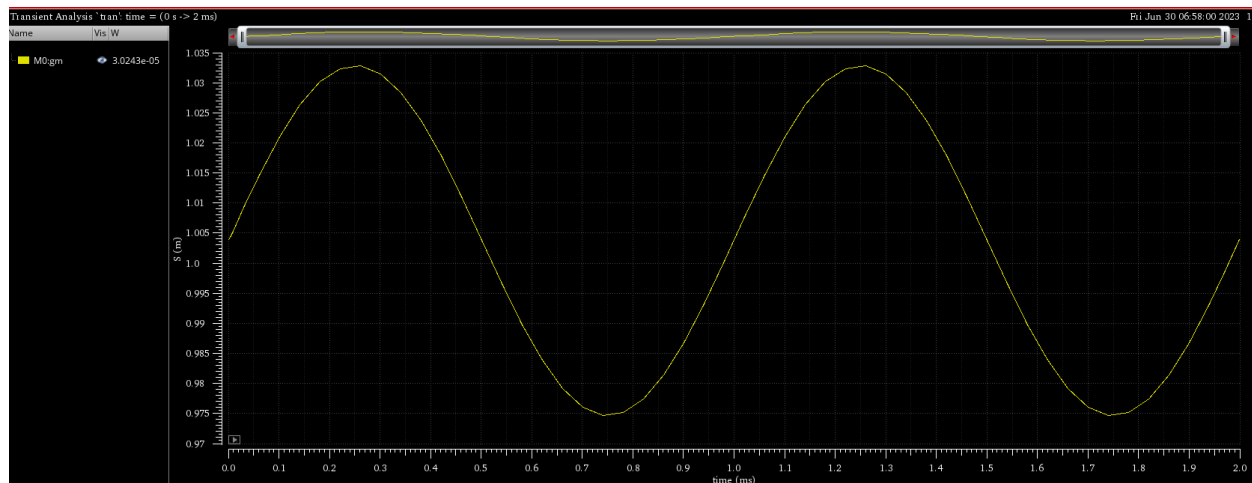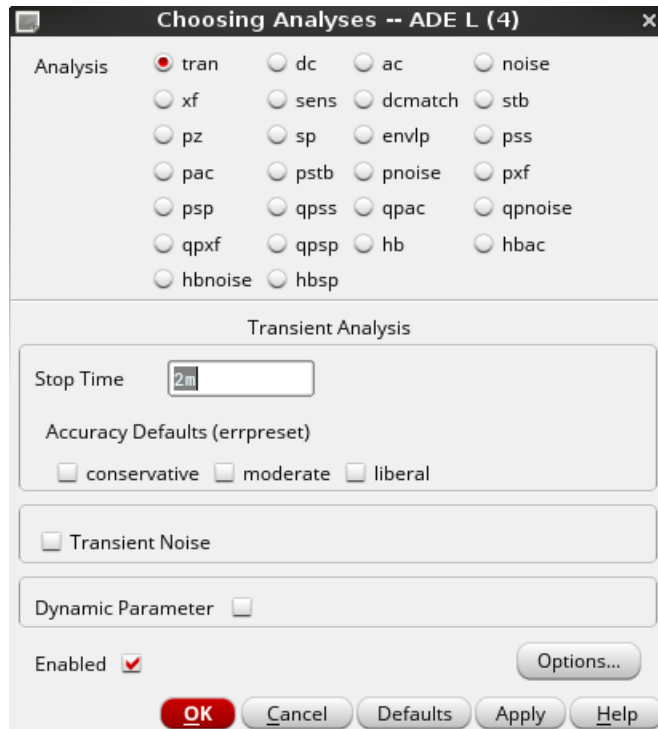- 5 CREATE A NEW SIMULATION CONFIGURATION. RUN TRANSIENT SIMULATION FOR 2MS. PLOT GM VS TIME. DOES GM VARY WITH THE INPUT SIGNAL? WHAT DOES THAT MEAN?



gm vs time

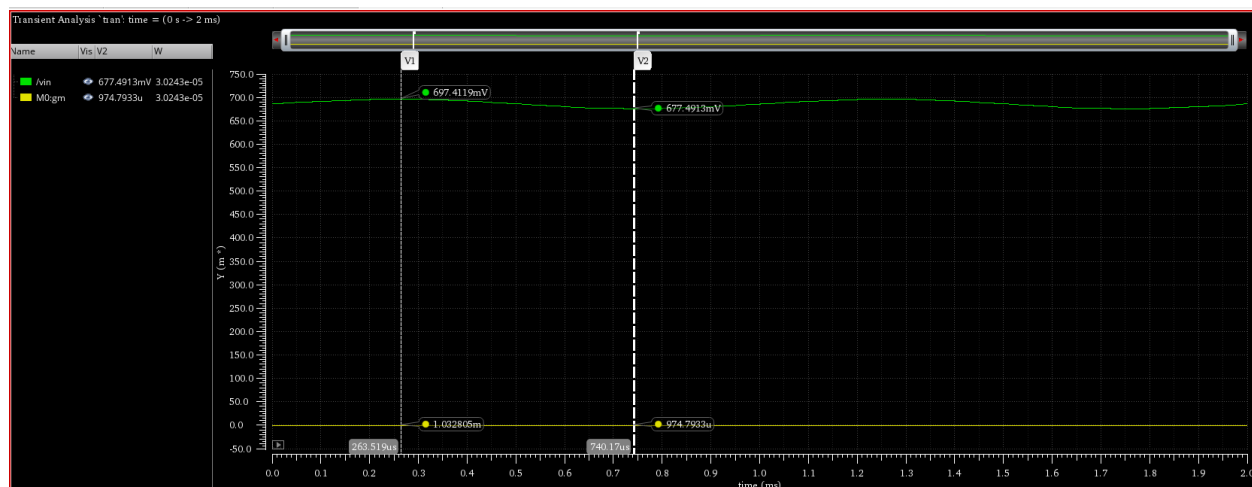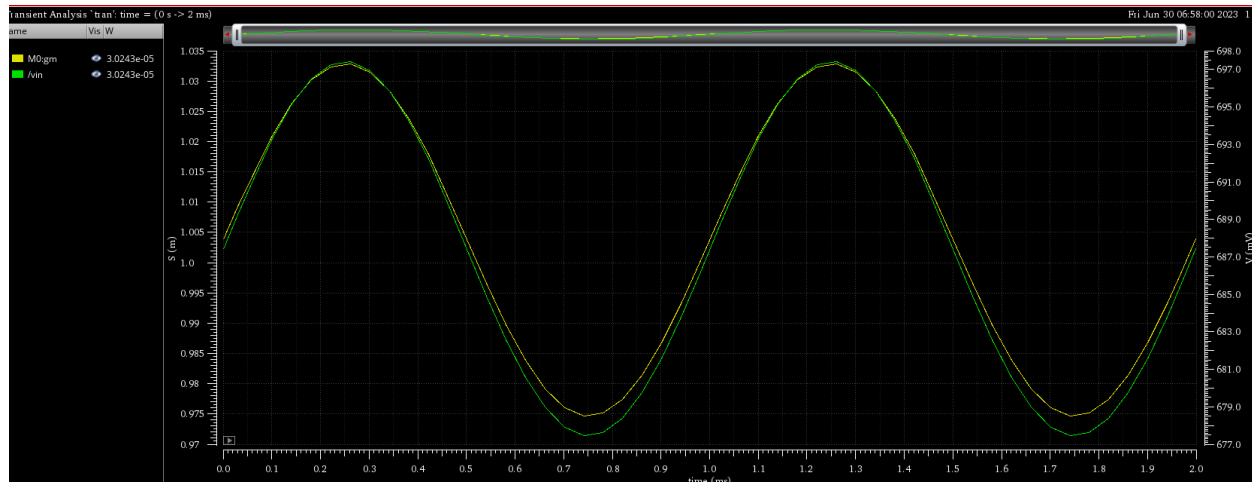

Yes, g_m varies with the input signal, as it is the slope of i_d vs V_{gs} (v_{in}), so when the input signal oscillates it changes g_m with it, **so the gain is not constant as gain = $g_m \cdot R_{out}$** , so the small signal linearization model is just an approximation as we consider g_m a constant, but that small error is actually acceptable as g_m change is very small and could be neglected.

6 IS THIS AMPLIFIER LINEAR? COMMENT.

NO, this amplifier is not linear because the gain is not constant but depends on V_{in} , because the gain depends on g_m and ($g_m = f(V_{in})$) and for linear gain, A_v should not be $f(V_{in})$ but we can solve it by increasing the source resistance.