
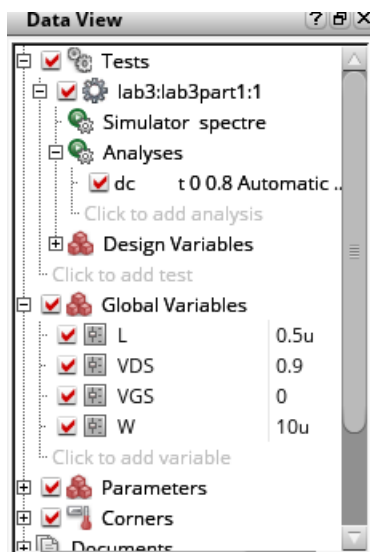


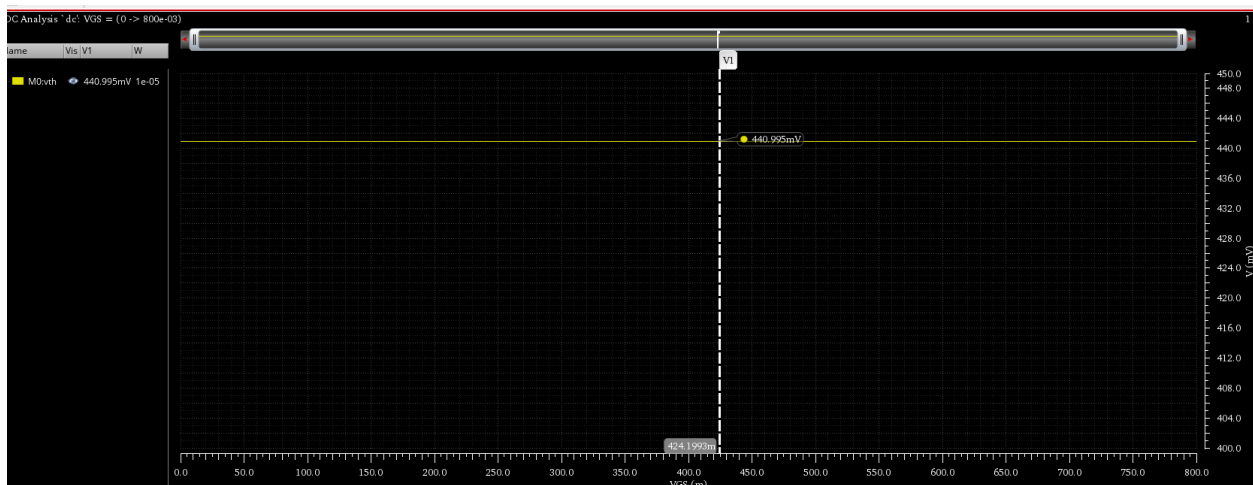PART 1: Sizing Chart

- 1 CREATE A TESTBENCH FOR NMOS TRANSISTOR AS SHOWN BELOW (WE WILL USE NMOS ONLY IN THIS LAB). USE $W = 10\mu m$ (WE WILL UNDERSTAND WHY SHORTLY) AND $L = 0.5\mu m$ (THE SAME L SELECTED BEFORE) .



- 2 SWEEP V_{GS} FROM 0 TO $\approx V_{TH} + 0.4V$ WITH 10mV STEP. SET $V_{DS} = V_{DD}/2$.



Vth for Nmos is $\sim 441\text{mV}$

We will sweep VGS from 0 to $\approx 0.4 + 0.441 = 0.841\text{V}$

Choosing Analyses -- ADE L (1)

Analysis: ☐ tran ☒ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☐ pz ☐ sp ☐ envlp ☐ pss
☐ pac ☐ pstb ☐ pnoise ☐ pxf
☐ psp ☐ qpss ☐ qpac ☐ qpnoise
☐ qpxf ☐ qpss ☐ hb ☐ hbac
☐ hbnoise ☐ hbsp

DC Analysis

Save DC Operating Point ☒
Hysteresis Sweep ☐

Sweep Variable

☐ Temperature
☒ Design Variable Variable Name:
☐ Component Parameter
☐ Model Parameter

Sweep Range

☒ Start-Stop Start: Stop:
☐ Center-Span


Sweep Type

☒ Step Size
☐ Number of Steps

Add Specific Points ☐


Enabled ☒

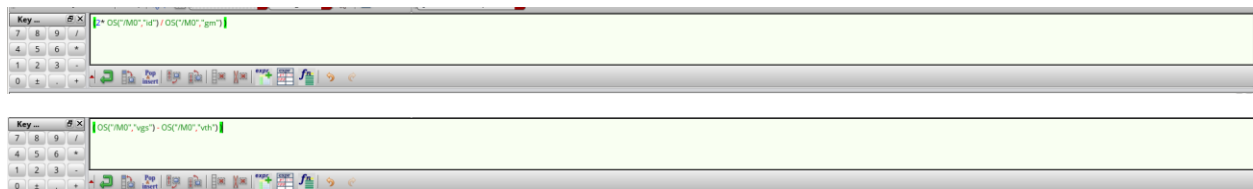- COMPARE $V^* = 2ID/gm$ AND $V_{ov} = V_{GS} - V_{TH}$ BY PLOTTING THEM OVERLAID. USE THE CALCULATOR TO CREATE EXPRESSIONS FOR V^* AND V_{ov} . EXPORT THE EXPRESSIONS TO ADEXL.




Test	Name	Type	Details	EvalType	Plot	Save	Spec	Weight	Units	Digits	Notation	Suffix
lab3:lab		signal		point	<input type="checkbox"/>	<input type="checkbox"/>						
lab3:...	V*	expr	((2 * OS("M0" "id")) / ...	point	<input checked="" type="checkbox"/>	<input type="checkbox"/>						
lab3:...	Vov	expr	(OS("M0" "vgs") - OS...	point	<input checked="" type="checkbox"/>	<input type="checkbox"/>						

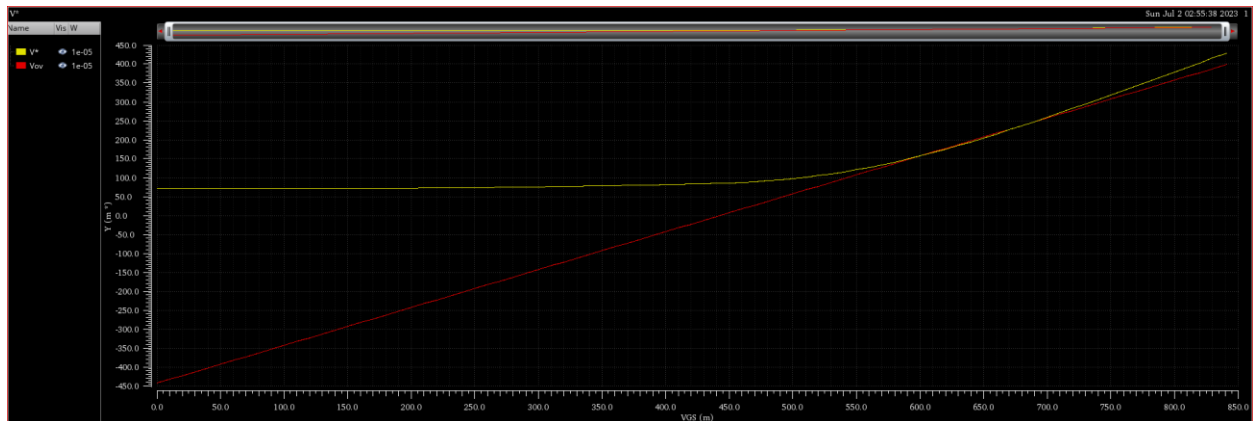- 4 PLOT V^* AND V_{ov} OVERLAID VS V_{GS} . MAKE SURE THE Y-AXIS OF BOTH CURVES HAS THE SAME RANGE.




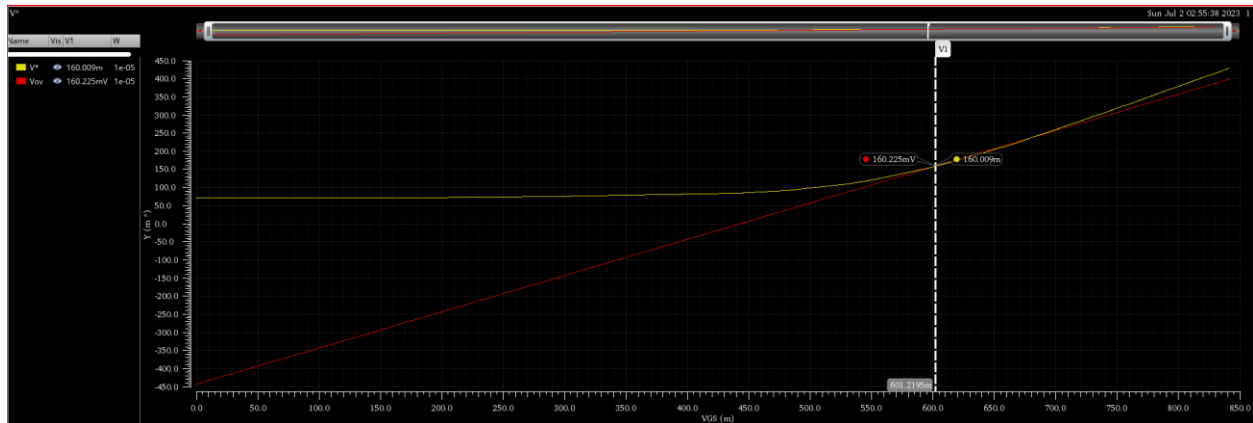
- 5 ON THE V^* AND V_{ov} CHART LOCATE THE POINT AT WHICH $V^* = V_{ov}$. FIND THE CORRESPONDING V_{ovQ} AND V_{GSQ} (USE $V^* = 160$ mV).



$$V_{ovq} = 160.225 \text{ m} \quad \&\& \quad V_{GSq} = 601.22 \text{ m}$$

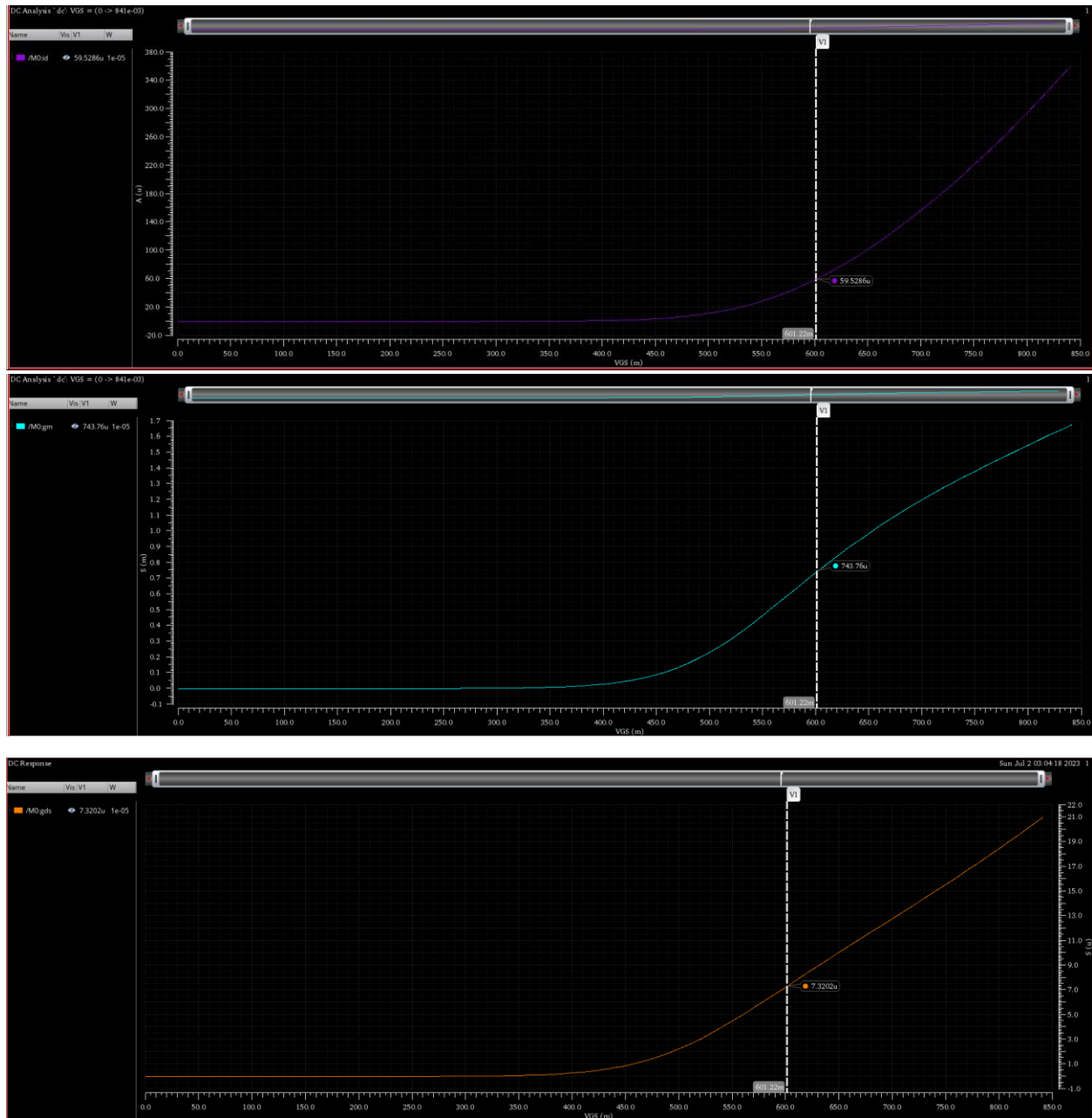6 PLOT ID , gm , AND gds VS VGS . FIND THEIR VALUES AT $VGSQ$. LET'S NAME THESE VALUES IDX , gmX , AND $gdsX$.



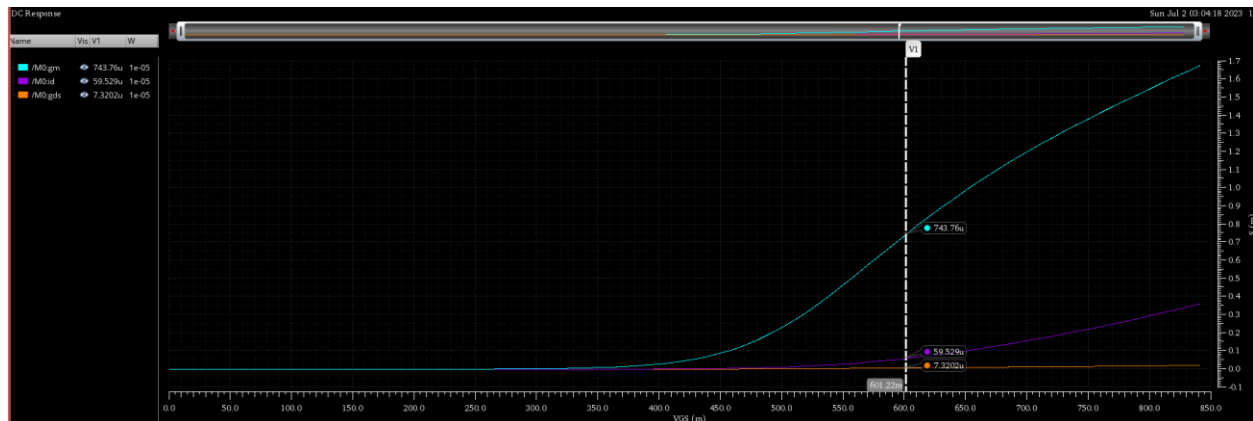

$$ID_X = 59.529 \text{ uA}, gm_X = 743.76 \text{ u}, gds_X = 7.3202 \text{ u}$$

7 CALCULATE **W**

$$W_{nmos} = \frac{10\text{u} * 15\text{u}}{59.529\text{u}} = 2.51978 \sim 2.52\text{u}$$

- Use $V^* = 160 \text{ mV}$ and $ID = 15 \text{ uA}$.

8 CALCULATE gm_Q AND gds_Q USING RATIO AND PROPORTION


$$gm_q(nmos) = \frac{2.52\text{u} * 743.76\text{u}}{10\text{u}} = 187.42\text{u}$$

$$gds_q(nmos) = \frac{2.52\text{u} * 7.3202\text{u}}{10\text{u}} = 1.844\text{u}$$

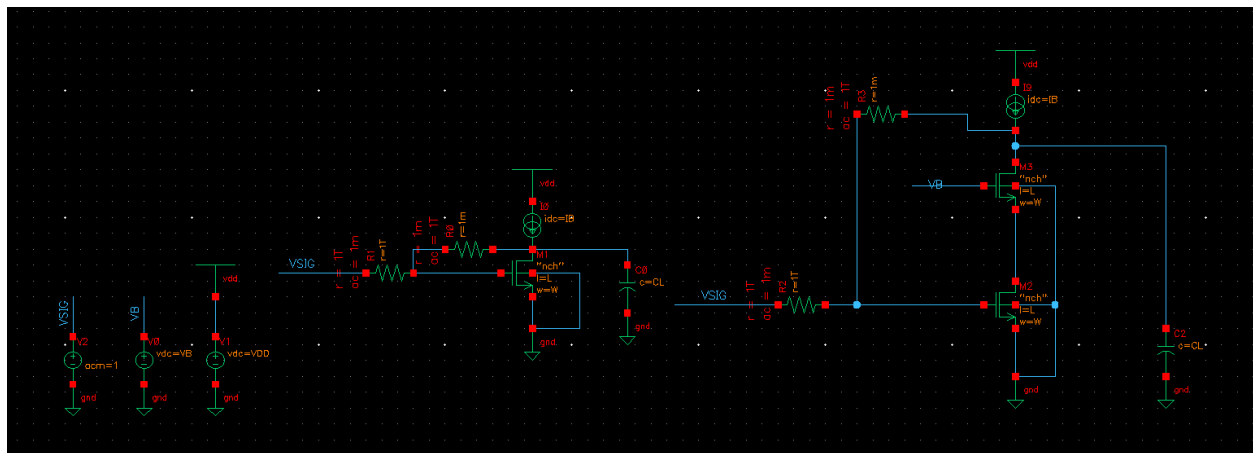PART 2: CS Amplifier

OP ANALYSIS


- 1 CREATE A NEW CELL AND SCHEMATIC. CONSTRUCT THE CIRCUIT SHOWN BELOW. USE $I_B = 20\ (15)\ \mu A$, $L = 0.5\ \mu m$, W AS SELECTED IN PART 1, AND $C_L = 1\ pF$. • Use $V^* = 160\ mV$ and $I_D = 15\ \mu A$.



Global Variables	
<input checked="" type="checkbox"/>	CL
<input checked="" type="checkbox"/>	IB
<input checked="" type="checkbox"/>	L
<input checked="" type="checkbox"/>	VB
<input checked="" type="checkbox"/>	VDD
<input checked="" type="checkbox"/>	W


1p
15u
0.5u
0
1.8
2.52u

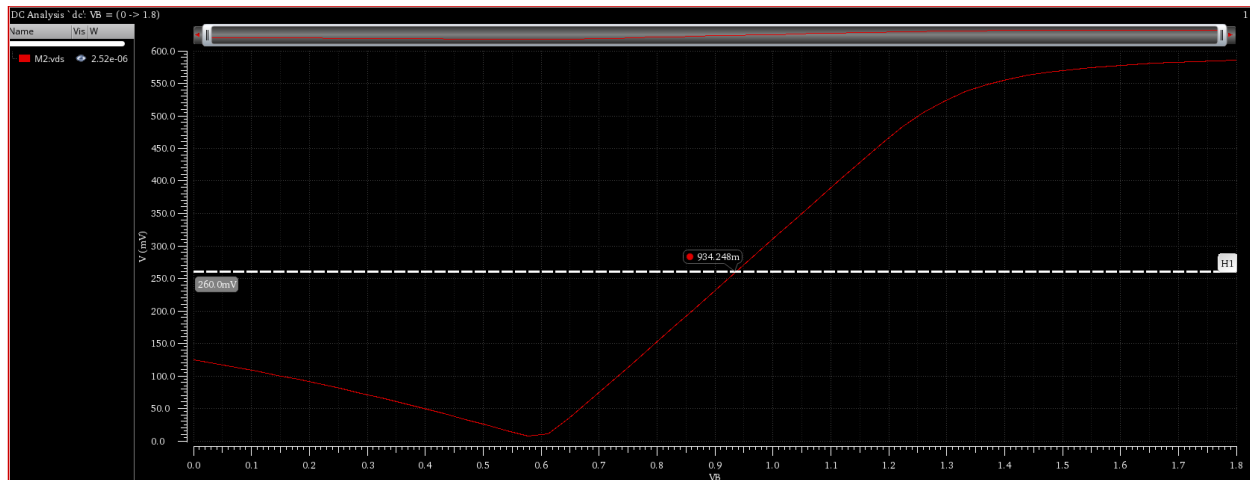- 2 CHOOSE V_B (THE CASCODE DEVICE BIAS VOLTAGE) SUCH THAT M2 HAS $V_{DS} \approx V^* + 100mV$ (YOU MAY SWEEP V_B AND PLOT V_{DS} VS V_B TO HELP YOU CHOOSE A GOOD VALUE FOR V_B).




$V_B = 934.248m$

3 BIAS TRANSISTORS IN SATURATION

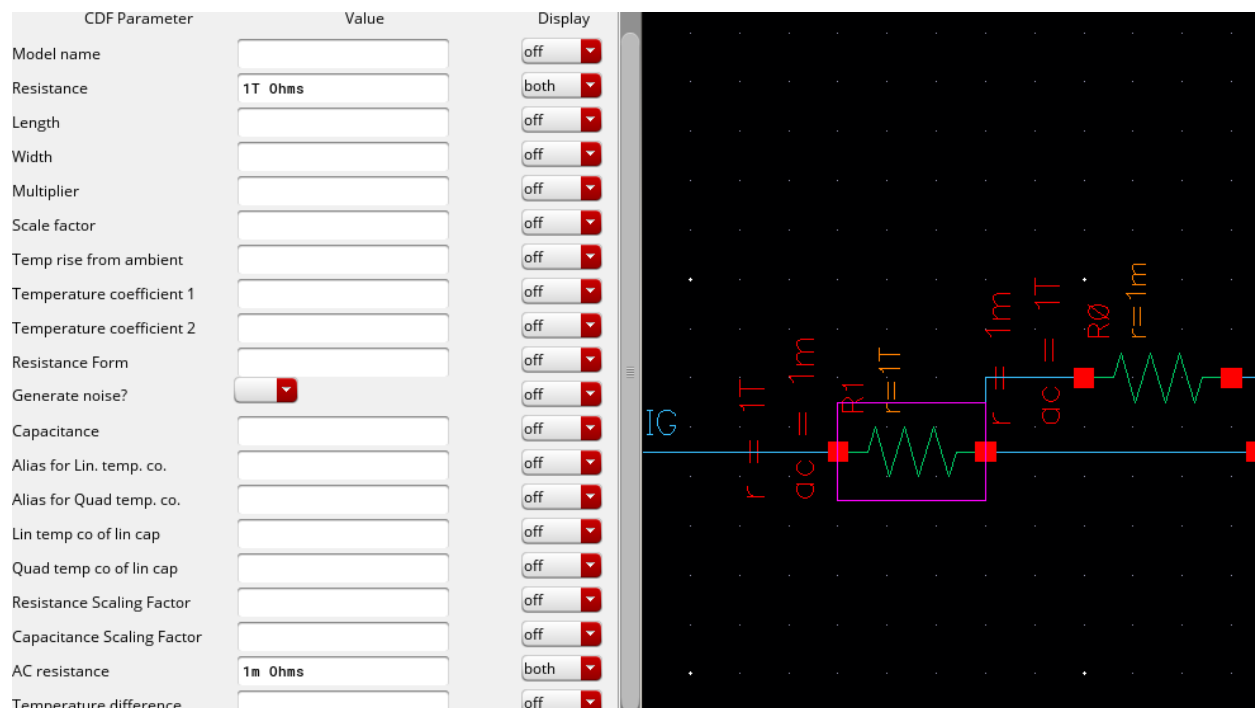

input resistance 1T DC and 1m AC

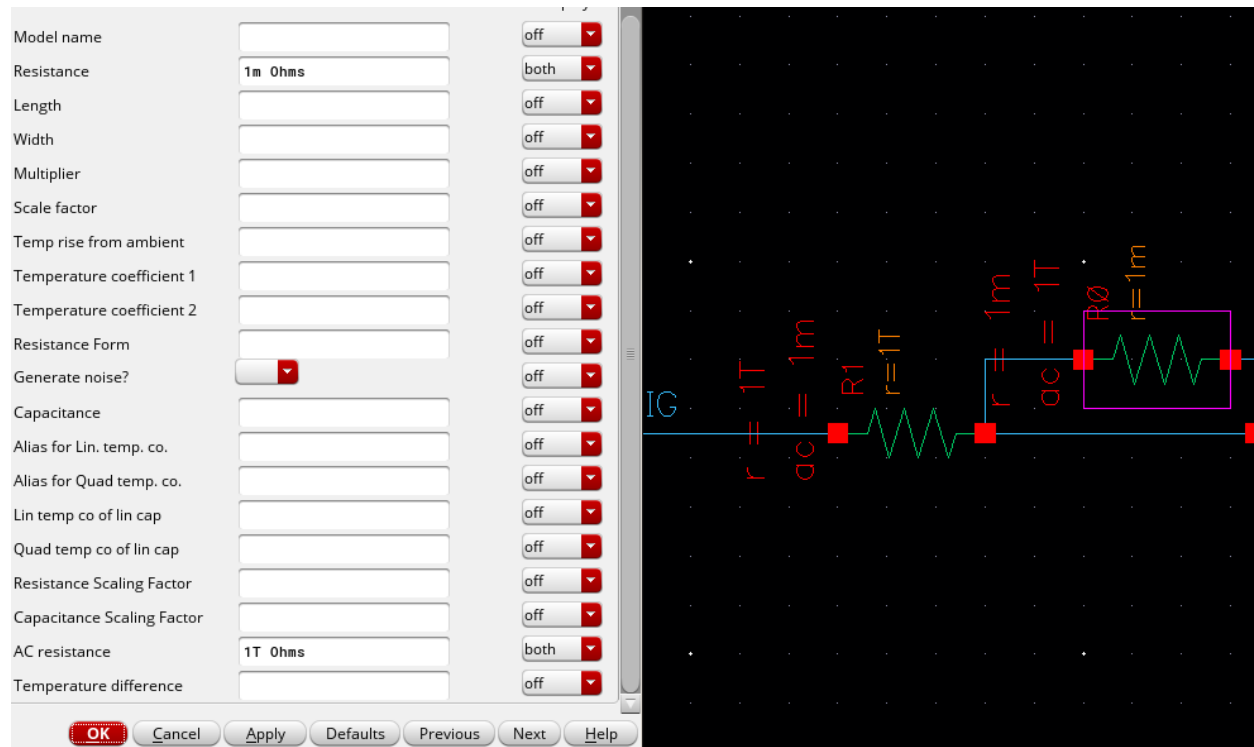


feedback resistance 1m DC and 1T AC

4 SIMULATE THE DC OP POINT OF THE ABOVE CS AND CASCODE AMPLIFIERS. REPORT A SNAPSHOT SHOWING THE FOLLOWING PARAMETERS FOR M1, M2 AND M3 IN ADDITION TO DC NODE VOLTAGES CLEARLY ANNOTATED


4.1 M1

lab3:lab3part2:1	ID_M1	15.01u			
lab3:lab3part2:1	VGS_M1	603.6m			
lab3:lab3part2:1	VDS_M1	603.6m			
lab3:lab3part2:1	VTH_M1	442.6m			
lab3:lab3part2:1	VDSAT_M1	127.1m			
lab3:lab3part2:1	GM_M1	187.3u			
lab3:lab3part2:1	GDS_M1	2.033u			
lab3:lab3part2:1	GMB_M1	51.14u			
lab3:lab3part2:1	CDB_M1	-2.076f			
lab3:lab3part2:1	CGD_M1	-1.191f			
lab3:lab3part2:1	CGS_M1	-9.007f			
lab3:lab3part2:1	CSB_M1	-4.46f			
lab3:lab3part2:1	Region_M1	2			

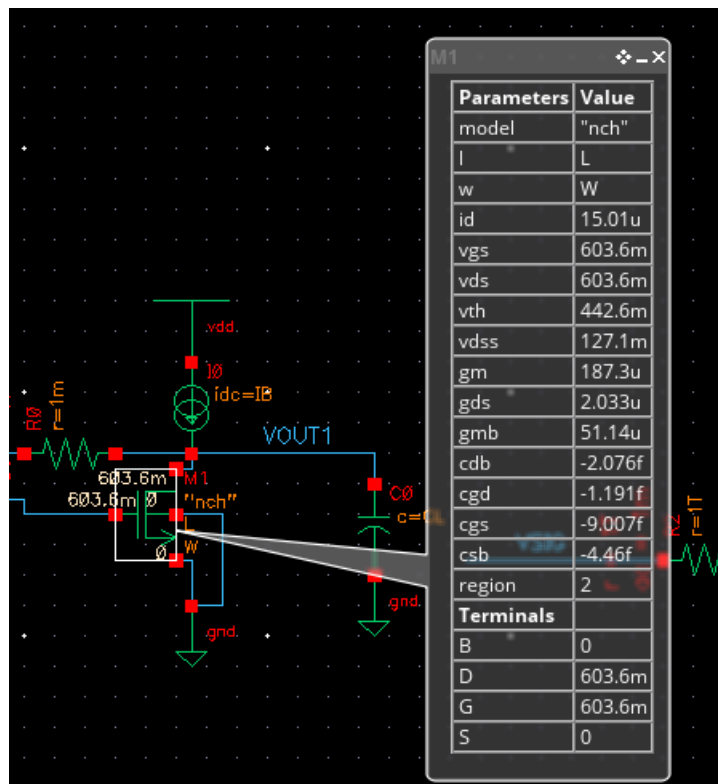


4.2 M2

lab3:lab3part2:1	ID_M2	15u			
lab3:lab3part2:1	VDS_M2	260m			
lab3:lab3part2:1	VTH_M2	445.1m			
lab3:lab3part2:1	VDSAT_M2	128.5m			
lab3:lab3part2:1	GM_M2	184.4u			
lab3:lab3part2:1	GDS_M2	3.926u			
lab3:lab3part2:1	GMB_M2	50.39u			
lab3:lab3part2:1	CDB_M2	-2.282f			
lab3:lab3part2:1	CGD_M2	-1.227f			
lab3:lab3part2:1	CGS_M2	-9.027f			
lab3:lab3part2:1	CSB_M2	-4.449f			
lab3:lab3part2:1	VGS_M2	608.2m			
lab3:lab3part2:1	Region_m2	2			

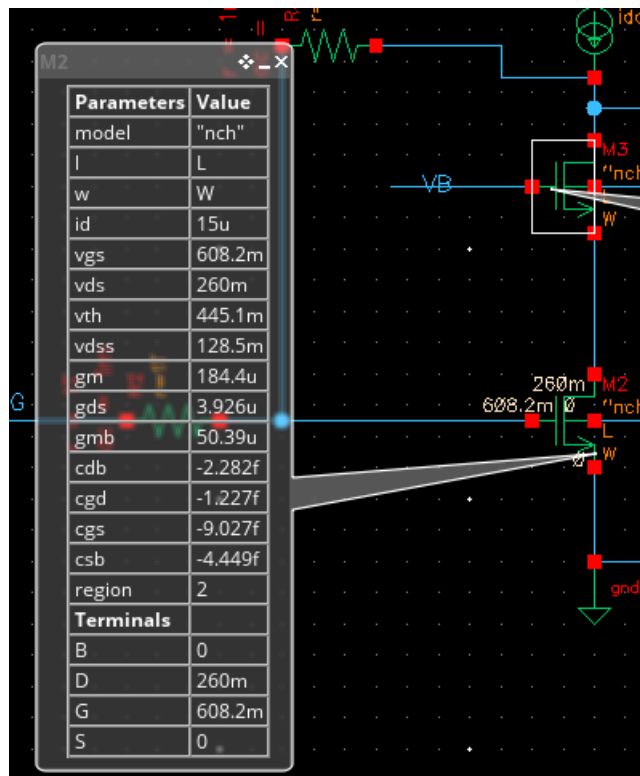

4.3 M3

lab3:lab3part2:1	ID_M3	15u			
lab3:lab3part2:1	VGS_M3	674.3m			
lab3:lab3part2:1	VDS_M3	348.2m			
lab3:lab3part2:1	VTH_M3	520m			
lab3:lab3part2:1	VDSAT_M3	130.8m			
lab3:lab3part2:1	GM_M3	188.3u			
lab3:lab3part2:1	GDS_M3	2.797u			
lab3:lab3part2:1	GMB_M3	46.69u			
lab3:lab3part2:1	CDB_M3	-2.086f			
lab3:lab3part2:1	CGD_M3	-1.202f			
lab3:lab3part2:1	CGS_M3	-8.951f			
lab3:lab3part2:1	CSB_M3	-4.015f			
lab3:lab3part2:1	Region_M3	2			

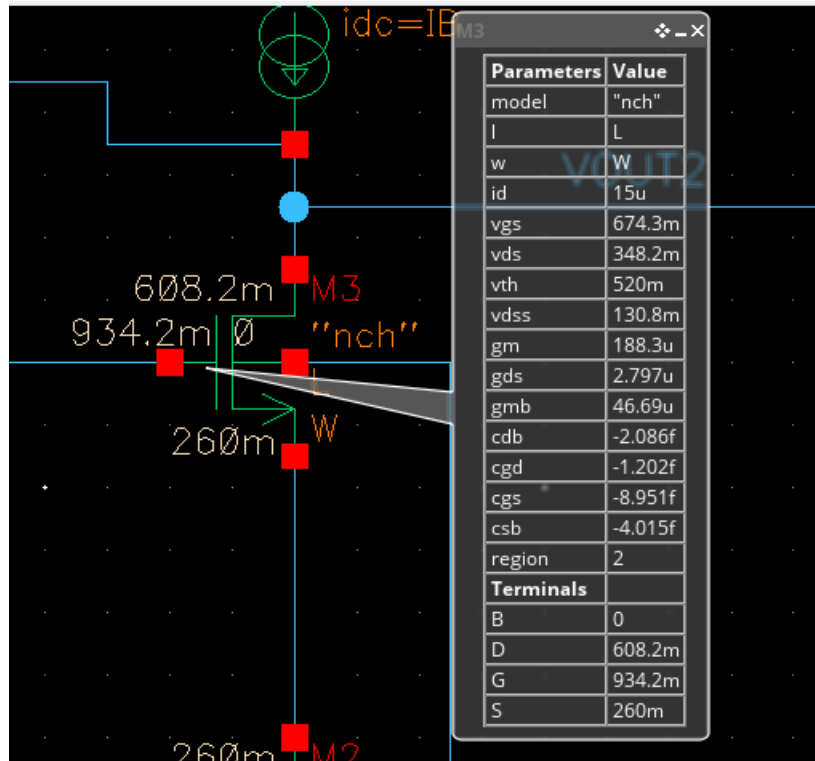

5 CHECK THAT ALL TRANSISTORS OPERATE IN SATURATION.

cc wcm

Cadence Hint: The "region" meaning is as follows: (0 cut-off, 1 triode, 2 sat, 3 subth, and 4 breakdown).

Region is 2 in the three transistors, so they are all in saturation, or we can analysis it:

M1 : $V_{ov} = V_{GS} - V_{TH} = 161\text{mV}$,, $V_{DS} = 603.6\text{mV}$ So: $V_{DS} > V_{ov}$ (SAT)

M2 : $V_{ov} = V_{GS} - V_{TH} = 163.1\text{mV}$,, $V_{DS} = 260\text{mV}$ So: $V_{DS} > V_{ov}$ (SAT)

M3: $V_{ov} = V_{GS} - V_{TH} = 154.3\text{mV}$,, $V_{DS} = 348.2\text{mV}$ So: $V_{DS} > V_{ov}$ (SAT)

6 DO ALL TRANSISTORS HAVE THE SAME V_{TH} ? WHY?

No, they don't have the same threshold voltage, because of body effect as they don't have the same V_{SB} .

7 WHAT IS THE RELATION (\ll , $<$, $=$, $>$, \gg) BETWEEN g_m AND g_{ds} ?

$g_m \gg g_{ds}$

8 WHAT IS THE RELATION (\ll , $<$, $=$, $>$, \gg) BETWEEN GM AND GMB?

gm $>$ gmb

9 WHAT IS THE RELATION (\ll , $<$, $=$, $>$, \gg) BETWEEN CGS AND CGD?

CGS $>$ CGD

10 WHAT IS THE RELATION (\ll , $<$, $=$, $>$, \gg) BETWEEN CSB AND CDB?

CSB $>$ CDB

WE TOOK ABSLUIITE VALUES

AC ANALYSIS

- 1 CREATE A NEW SIMULATION CONFIGURATION. PERFORM AC ANALYSIS (1Hz:10GHz, LOGARITHMIC, 10POINTS/DECADE) TO SIMULATE GAIN AND BANDWIDTH.

Choosing Analyses - ADE L (7)

Analysis

<input type="radio"/> tran	<input type="radio"/> dc	<input checked="" type="radio"/> ac	<input type="radio"/> noise
<input type="radio"/> xf	<input type="radio"/> sens	<input type="radio"/> dcmatch	<input type="radio"/> stb
<input type="radio"/> pz	<input type="radio"/> sp	<input type="radio"/> envlp	<input type="radio"/> pss
<input type="radio"/> pac	<input type="radio"/> pstb	<input type="radio"/> pnoise	<input type="radio"/> pxf
<input type="radio"/> psp	<input type="radio"/> qpss	<input type="radio"/> qpac	<input type="radio"/> qpnoise
<input type="radio"/> qpxf	<input type="radio"/> qpzp	<input type="radio"/> hb	<input type="radio"/> hbac
<input type="radio"/> hbnoise	<input type="radio"/> hbzp		

AC Analysis

Sweep Variable

☒ Frequency

☐ Design Variable

☐ Temperature

☐ Component Parameter

☐ Model Parameter

☐ None

Sweep Range

☒ Start-Stop

Start Stop

☐ Center-Span

Sweep Type

Logarithmic ☒

☒ Points Per Decade

☐ Number of Steps

Add Specific Points ☐

2 USE CALCULATOR TO CREATE EXPRESSIONS FOR CIRCUIT PARAMETERS (DC GAIN, BW, GBW, AND UGF) AND EXPORT THEM TO ADEXL.

lab3:lab3part2:1	dB20(VF("/VOUT1"))				
lab3:lab3part2:1	ymax(dB20(VF("/VOUT1")))	39.29			
lab3:lab3part2:1	ymax(mag(VF("/VOUT1")))	92.13			
lab3:lab3part2:1	bandwidth(VF("/VOUT1") 3 "I...	322k			
lab3:lab3part2:1	gainBwProd(VF("/VOUT1"))	29.74M			
lab3:lab3part2:1	dB20(VF("/VOUT2"))				
lab3:lab3part2:1	ymax(dB20(VF("/VOUT2")))	72.03			
lab3:lab3part2:1	ymax(mag(VF("/VOUT2")))	3.993k			
lab3:lab3part2:1	bandwidth(VF("/VOUT2") 3 "I...	7.211k			
lab3:lab3part2:1	gainBwProd(VF("/VOUT2"))	28.86M			

lab3:lab3part2:1	unityGainFreq(VF("/VOUT1"))	30M			
lab3:lab3part2:1	unityGainFreq(VF("/VOUT2"))	29.13M			

3 REPORT THE BODE PLOT (MAGNITUDE) OF CS AND CASCODE APPENDED ON THE SAME PLOT



4 USING SMALL SIGNAL PARAMETERS FROM OP SIMULATION, PERFORM HAND ANALYSIS TO CALCULATE DC GAIN, BW, AND GBW OF BOTH CIRCUITS.

- Ignore any requirement in the lab regarding the "analytical" calculation of the frequency response parameters.

In CS : dc gain $= g_m \cdot r_o = \frac{g_m}{g_{ds}} = \frac{187.3 \mu}{2.033 \mu} = 92.13$

Subject: موضوع الدرس Date: التاريخ

$V_{gs} = V_{in}$

$V_{bs} = 0$

$I_{s.c}$

$|A_v| = G_m R_{out}$

$G_m = \frac{I_{s.c}}{V_{in}}$

Kcl @ D: $I_{s.c} = -V_{in} g_m$, $\frac{I_{s.c}}{V_{in}} = -g_m$

$G_m = -g_m$

$R_{LD} \Rightarrow R_{out} = r_o // \infty = r_o$

$|A_v| = g_m r_o = \frac{g_m}{g_{ds}} = \frac{187.3 \mu}{2.033 \mu}$

$= 92.13$

Ebalem

In Cascode : dc gain = Rout * GM

$$R_{OUT} = r_{o3}(1 + (g_{m3} + g_{m_{b3}}) * r_{o2}) = \frac{1}{2.797u} (1 + (188.3u + 46.69u) * \frac{1}{3.926u}) = 21.757 \frac{1}{u}$$

$$GM = -g_{m2} = -184.4u$$

$$|Dc\ gain| = GM * R_{OUT} = 184.4 * 21.757 = 4012$$

Subject: موضوع الدرس

Date: التاريخ

$$R_{out} = \frac{V_o}{V_{in=0}} = \frac{V_{o3} (1 + (g_{m3} + g_{m_{b3}}) V_{o2})}{V_{in=0}}$$

$$I_{sc} = -V_{in} (g_{m2})$$

$$G_m = \frac{I_{sc}}{V_{in}} = - (g_{m2})$$

$$|A_v| = g_{m2} V_{o3} (1 + (g_{m3} + g_{m_{b3}}) V_{o2})$$

$$= 184.4 \times \frac{1}{2.797} \times \frac{1 + (188.3 + 46.69) \times \frac{1}{3.926}}{1} = 4012$$

5 REPORT A TABLE COMPARING THE DC GAIN, BW, UGF, AND GBW OF BOTH CIRCUITS FROM SIMULATION AND HAND ANALYSIS.

lab3:lab3part2:1	unityGainFreq(VF("/VOUT1"))	30M			
lab3:lab3part2:1	unityGainFreq(VF("/VOUT2"))	29.13M			

	Simulation		hand analysis.	
	CS	Cascode	CS	Cascode
DC GAIN	92.13	3993	92.13	4012
BW	322k	7.211k		
UGF	30M	29.13M		
GBW	29.74M	28.86M		

6 COMMENT ON THE RESULTS.

Dc gain in Cascode is much bigger than the gain in CS as it boosts Rout (Gm isn't boosted), and if we compared the hand analysis with the simulation results, we will see they are almost the same (error less than 1%).

Bw cs >> BW cascode , UGF cs > UGF cascode , GBW cs > GBW cascode.