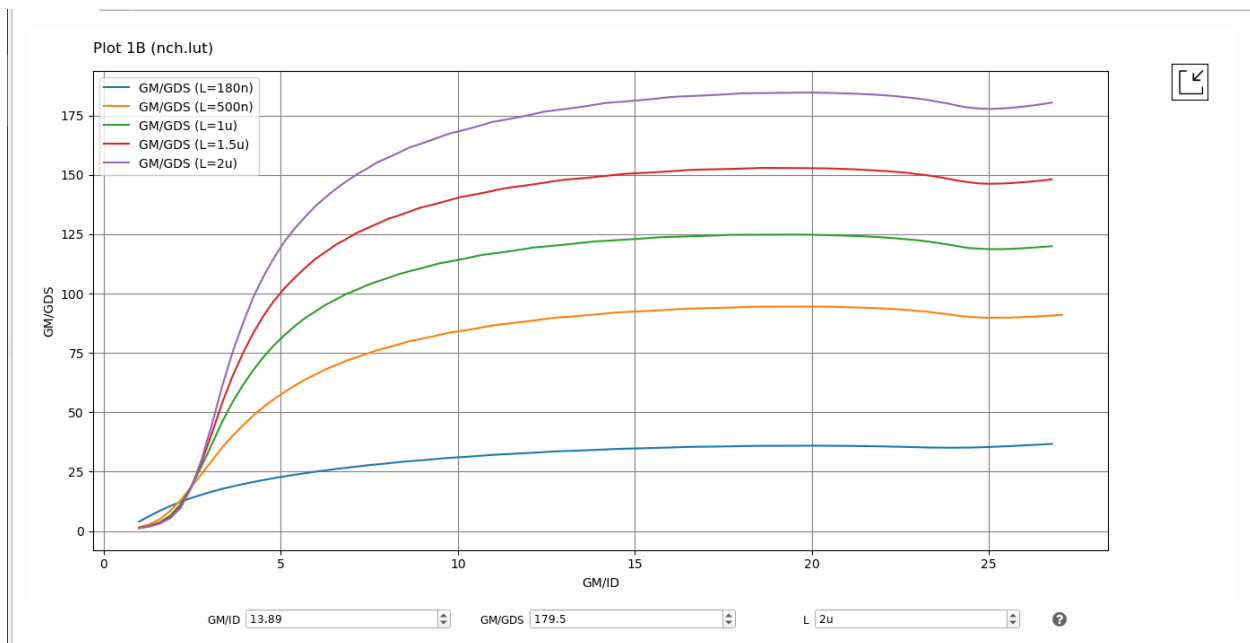



Part1

- 1 USING ADT DEVICE XPLORE, PLOT THE FOLLOWING DESIGN CHARTS VS GM/ID FOR BOTH PMOS AND NMOS. SET $V_{DS} = V_{DD}/3$ AND $L = 0.18\mu, 0.5\mu, 1\mu, 2\mu$


1.1 GM/G_{DS} NMOS




PMOS

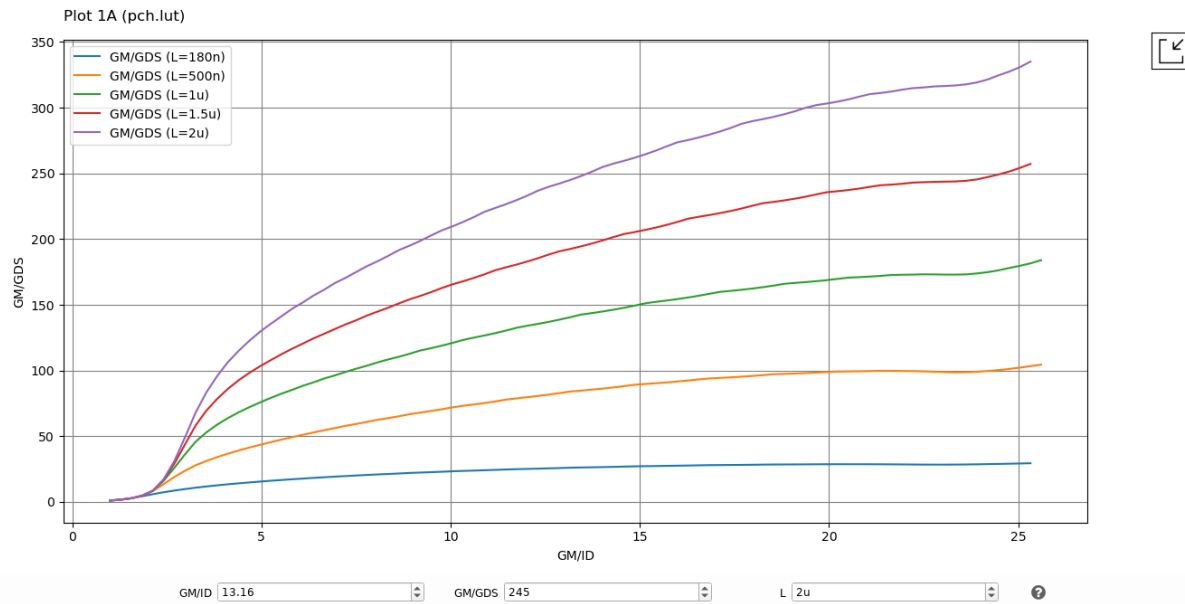


1.2 ID/W NMOS

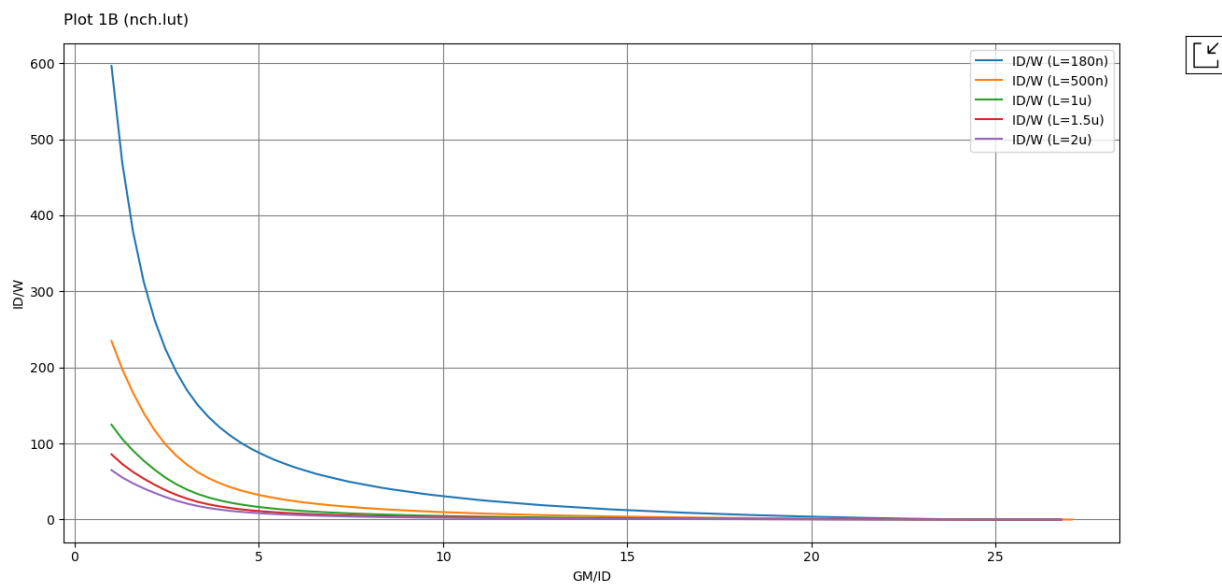


PMOS

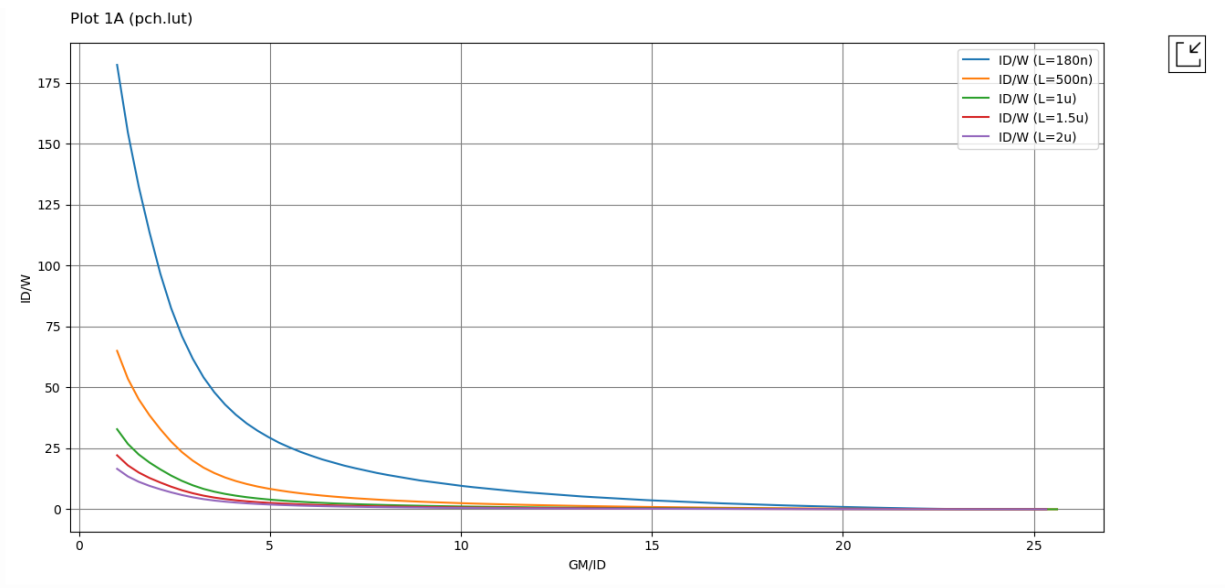

1.3 GM/CGG NMOS

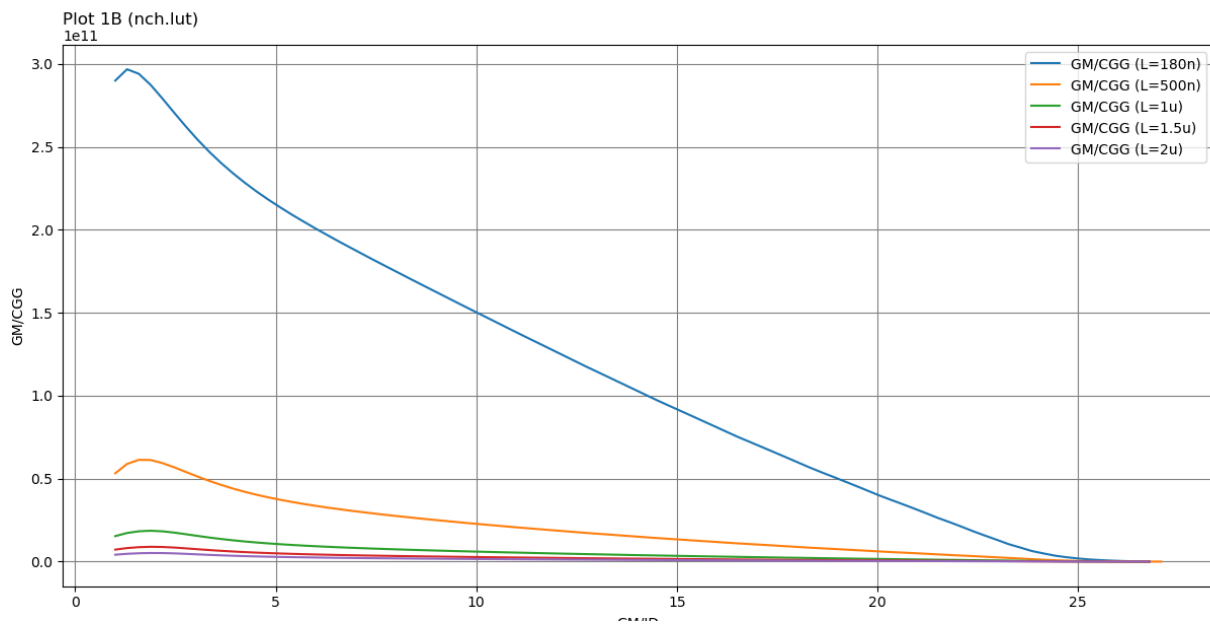


PMOS

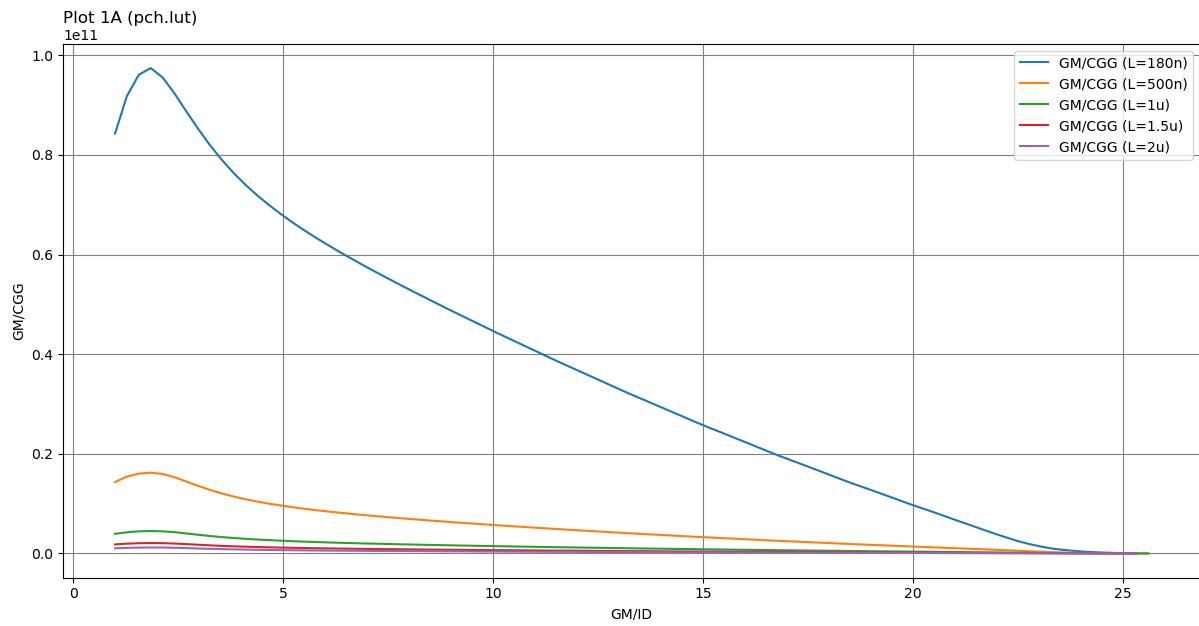


1.4 VGS

Nmos

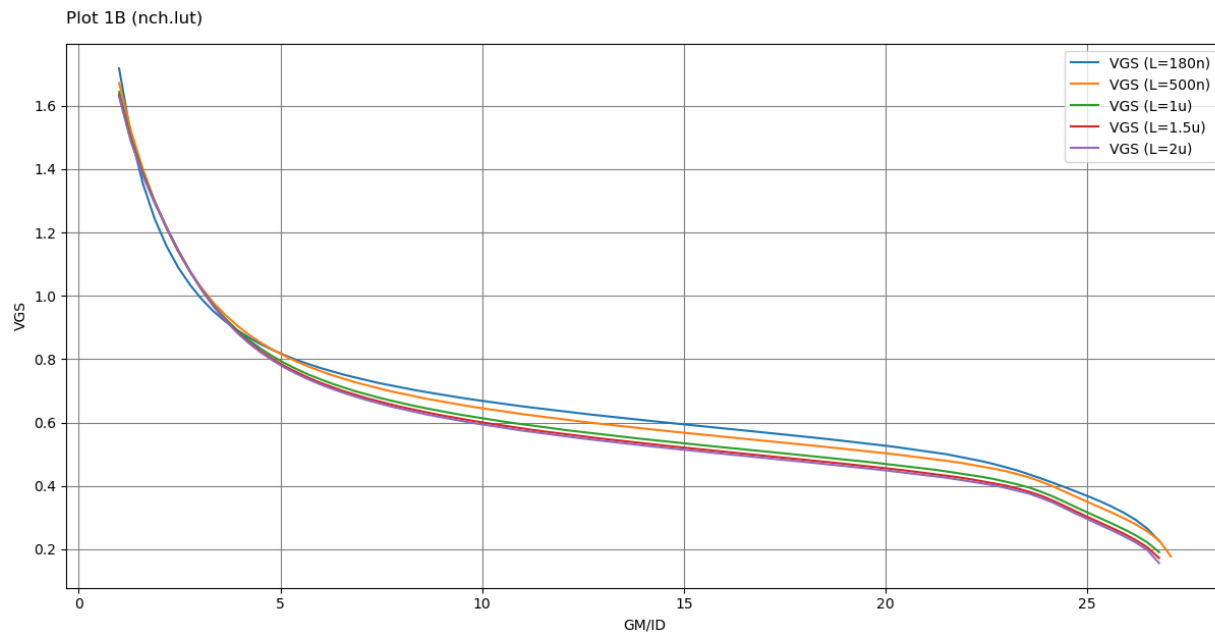


PMOS

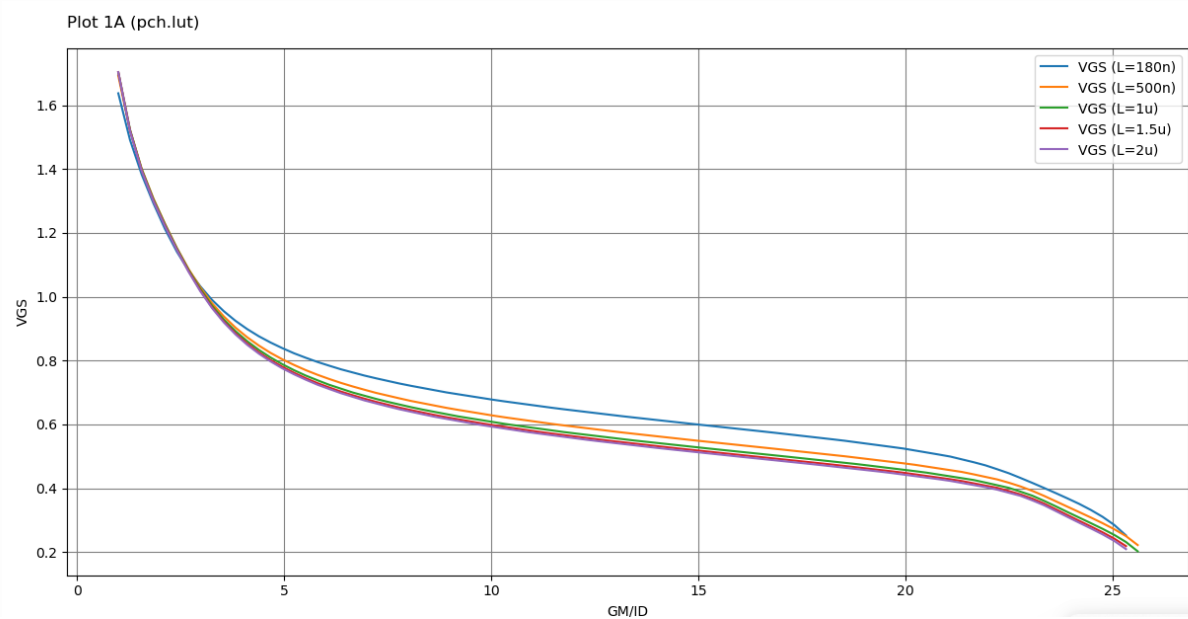


PART2: OTA Design

1 DETAILED DESIGN PROCEDURE AND HAND ANALYSIS. JUSTIFY WHY YOU USED NMOS OR PMOS INPUT PAIR FOR EACH STAGE

1.1 INPUT PAIR

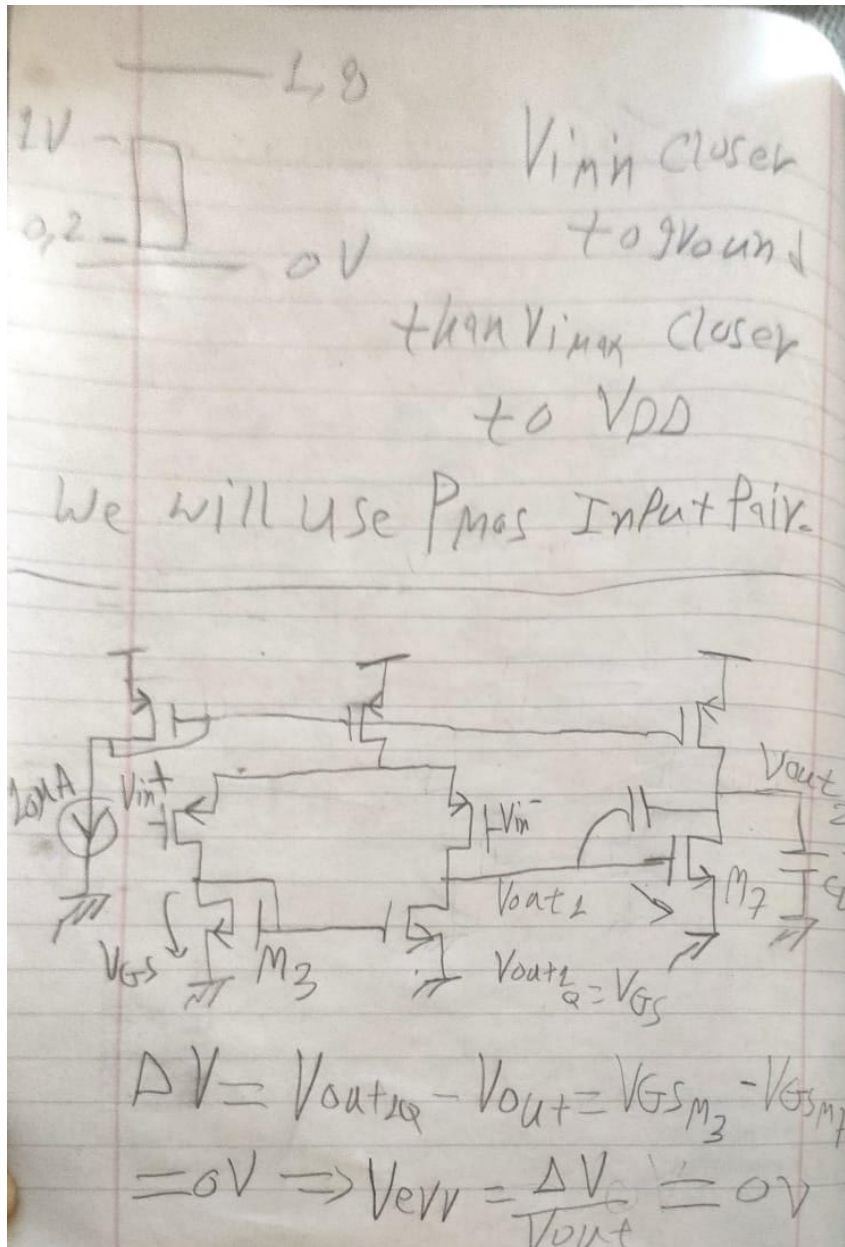

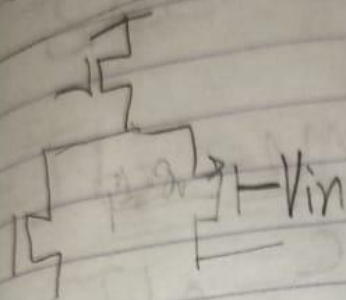To minimize the error we
choiced the 2nd stage to
be NMOS Input.



We will neglect body effect $V_{bs}=0$

$$\text{and } V_{DS} = \frac{V_{DD}}{3} = 0,5V$$

$$t_{rise} = 2,2 \tau \leq 70ns$$

$$RC \leq 31,8ns$$

$$\frac{1}{RC} \geq 31,4 \mu V/d/s$$

Assuming $C_C = \frac{C_L}{2} = 2,5 \text{ pF}$

$$\frac{G_m}{C_C} \geq 31,4 \text{ M}$$

$$(G_{m_{I/P}} \geq 78,5 \mu\text{S})$$

$$(G_m = 80)$$

$\therefore \text{Slewrate} = 5, \quad I_{b1} = 5 \times 2,5$
 $= 12,5 \mu\text{A}$

$$I_{b2} = 60 - 12,5 = 47,5 \mu\text{A}$$

$$\left(\frac{I_m}{I_{I/P}} \right) \geq \frac{80}{\frac{12,5}{2}} \geq 12,8$$

$$\left(\frac{I_{CT+U91} - I_{\text{Ideal}}}{I_{\text{Ideal}}} \right) \times 100 \geq 0,05$$

$$\frac{I}{A_{ol}} \geq 5 \times 10^{-4}$$

$$A_{OL} = 2000 = 66 \text{ dB}$$

$$A_{OL \text{ first}} = 36 \text{ dB}, A_{OL \text{ second}} = 30 \text{ dB}$$

$$\frac{g_m V_o}{2} = 63,1 \Rightarrow \left(\frac{g_m}{g_{DS}} \right)_{IP} = 126,2$$

So for I/P $I_D = 6,25 \mu\text{A}$,

$$V_{DS} = 0,6, V_{GB} = 1,2$$

$$\left(\frac{g_m}{I_D} \right) = 12,8 - \left(\frac{g_m}{g_{DS}} \right) = 126,2$$

ADT Sizing Assistant

Settings

Help

LUT Settings

LUTs Directory

:/user01/projects/ex_LUTs/

LUT

pch

Corner

tt

Temp (°C)

27.0

State1

Save State

ID

6.25u

gm/ID

12.8

gm/gds

126.2

VDS

0.6

VSb

0

Stack

1

Get

Apply

Y-Expr

gm

Plot

Replace

Append

Device Parameters

#	Parameter	Value
1	ID	6.25u
2	L	890n
3	W	8.22u
4	VGS	565.2m
5	VDS	600m
6	VSb	0
7	gm/ID	12.54
8	Vstar	159.5m
9	fT	223.4M
10	gm/gds	125.5
11	VA	10.01
12	ID/W	760.3m
13	gm/W	9.536
14	AREA	7.316p
15	gm	78.39u

ADT Sizing Assistant

Settings

Help

LUT Settings

LUTs Directory

:/user01/projects/ex_LUTs/

LUT

pch

Corner

tt

Temp (°C)

27.0

State1

Save State

ID

6.25u

gm/ID

12.8

gm/gds

126.2

VDS

0.6

VSb

0

Stack

1

Get

Apply

Y-Expr

gm

Plot

Replace

Append

Device Parameters

#	Parameter	Value
16	gmb	24.12u
17	gds	624.4n
18	ro	1.602M
19	VTH	413.2m
20	VDSAT	127m
21	cgg	55.85f
22	cgs	47.7f
23	cgd	5.232f
24	cgb	2.918f
25	cdb	8.99f
26	csb	22.79f
27	idnth2	1.144e-24
28	vgnth2	186.1e-18
29	idnfl2	13e-21
30	vgnfl2	2.116p

1.2 2ND STAGE INPUT

Second Stage Input M_8

$$W_{P2} = 4 \mu s \Rightarrow \frac{g_{m2}}{C_L} = 4 \frac{g_{m1}}{C_C}$$

$$\frac{g_{m8}}{C_C} = 4 \times \frac{80}{0,5 \mu s}$$

$$g_{m8} = 640 \mu S$$

2nd Stage $g_{in} = 30 dB = 31,62$

$$\frac{g_m}{29 \mu s} = 31,62 \Rightarrow \left(\frac{g_m}{29 \mu s} \right)_8 = 63,24$$

$$\approx 63,3$$

$$V_{DS} = 0,9, V_{GB} = 0, I_{D2} = 47,5 \mu A$$

ADT Sizing Assistant

Settings

Help

LUT Settings

LUTs Directory

⚙

⋮

⚙

⋮

LUT

nch

Corner

tt

Temp (°C)

27.0

State1

⚙

Save State

ID

⚙

47.5u

gm

⚙

640u

gm/gds

⚙

63.3

VDS

⚙

0.9

VGB

⚙

0

Stack

1

Get

Apply

Y-Expr

gm

Plot

Replace

Append

Device Parameters

#	Parameter	Value
1	ID	47.5u
2	L	280n
3	W	4.8u
4	VGS	607.2m
5	VDS	900m
6	VSb	0
7	gm/ID	13.28
8	Vstar	150.6m
9	fT	7.877G
10	gm/gds	61.73
11	VA	4.649
12	ID/W	9.896
13	gm/W	131.4
14	AREA	1.344p
15	gm	630.7u

ADT Sizing Assistant

Settings

Help

LUT Settings

LUTs Directory

⚙

⋮

⚙

⋮

LUT

nch

Corner

tt

Temp (°C)

27.0

State1

⚙

Save State

ID

⚙

47.5u

gm

⚙

640u

gm/gds

⚙

63.3

VDS

⚙

0.9

VGB

⚙

0

Stack

1

Get

Apply

Y-Expr

gm

Plot

Replace

Append

Device Parameters

#	Parameter	Value
16	gmb	158.8u
17	gds	10.22u
18	ro	97.87k
19	VTH	466.2m
20	VDSAT	114.8m
21	cgg	12.74f
22	cgs	9.828f
23	cgd	2.232f
24	cgb	683.6e-18
25	cdb	5.425f
26	csb	8.313f
27	idnth2	8.838e-24
28	vgnth2	22.22e-18
29	idnfl2	10.08e-18
30	vgnfl2	25.33p

1.3 MIRROR LOAD

For Mirror load

We got f_{Vom} SQ 1 $\sqrt{g_{m1} = 607,2 \mu A/V}$
2nd input stage

and gain is same f_{Vo} 1st stage
input, so $\left(\frac{g_m}{g_{ds}} = 126,2 \right)$

$I_D = 6,25$, $V_{DS} = 9,6$, $V_{GB} = 0$

ADT Sizing Assistant

Settings

Help

LUT Settings

LUTs Directory

:/user01/projects/ex_LUTs/

...

LUT

nch

Corner

tt

Temp (°C)

27.0

State1

Save State

ID

6.25u

VGS

607.2m

gm/gds

126.2

VDS

VGS

VGB

0

Stack

1

Get

Apply

Y-Expr

gm

Plot

Replace

Append

Device Parameters

#	Parameter	Value
1	ID	6.241u
2	L	1.22u
3	W	1.63u
4	VGS	607.2m
5	VDS	607.2m
6	VSb	0
7	gm/ID	9.911
8	Vstar	201.8m
9	ft	655.2M
10	gm/gds	125.9
11	VA	12.7
12	ID/W	3.829
13	gm/W	37.95
14	AREA	1.989p
15	gm	61.85u

ADT Sizing Assistant

Settings

Help

LUT Settings

LUTs Directory

:/user01/projects/ex_LUTs/

...

LUT

nch

Corner

tt

Temp (°C)

27.0

State1

Save State

ID

6.25u

VGS

607.2m

gm/gds

126.2

VDS

VGS

VGB

0

Stack

1

Get

Apply

Y-Expr

gm

Plot

Replace

Append

Device Parameters

#	Parameter	Value
16	gmb	16.85u
17	gds	491.3n
18	ro	2.035M
19	VTH	397.5m
20	VDSAT	157.4m
21	cgg	15.03f
22	cgs	13.42f
23	cgd	747.4e-18
24	cgb	862.7e-18
25	cdb	1.932f
26	csb	5.631f
27	idnth2	875.1e-27
28	vgnth2	228.8e-18
29	idnfl2	43.12e-21
30	vgnfl2	11.27p

1.4 THE TAIL

for the tail:

$$I = 12.5 \mu$$

$$C_{mir_{High}} = V_{DD} - V_{GS_{F/D}} - V_{Tail}^*$$

$$V_{Tail_{max}}^* = 1.8 - 1 - 0.5652 = 234.8 \text{ mV}$$

$\Rightarrow V^*$ for the Tail current

Source is the same for

2nd stage load, so to keep

the swing we will take

$$V^* = 1.8 - 1.6 = 0.2 \text{ V} \quad [299 \text{ mV}]$$

$$C_{MRR} \geq 74 \text{ dB}, C_{MRR} = 36 - A_{vcm}$$

$$A_{vcm} \leq -38 \text{ dB}$$

$$A_{vcm} \leq 0,125$$

$$\frac{1}{2 g_{m_{\text{mirror}}} Y_{o_{\text{Tail}}}} = 0,125$$

$$\frac{1}{Y_{o_{\text{Tail}}}} \geq g_{ds} = 1,55 \mu\text{S}$$

$$V_{DS} = 0,6, V_{SB} = 0$$



1.5 VERIFY THAT YOUR GM/ID CHOICES DO NOT VIOLATE THE CMIR AND THE PEAK-TO-PEAK OUTPUT SWING.

$C_{mir} LOW$

$$C_{mir} LOW = -|V_{GS2}| + |V_A| + V_{GS2}$$

$$200m = -701.2m + 160m + V_{GS2}$$

$$\boxed{V_{GS2} = 696.2} \quad \text{We didn't violate the } C_{MRR}$$

~~We found V_A (50mV) where~~
 V_A 2nd input = 150.6mV

So the output swing low


is NOT Violated.

$$R_Z = 1/g_{m2} \text{input (from sa)} = 1/630.7u$$



2 A TABLE SHOWING W , L , gm , ID , gm/ID , $vdsat$, $Vov = VGS - VTH$, AND $V^* = 2ID/gm$ OF ALL TRANSISTORS (AS CALCULATED FROM SA).

TRANS	W	L	GM	ID	GM/ID	VDSsat	VOV	VSTAR
Input pair	8.22u	890n	78.39u	6.25u	12.54	127m	152m	159.5m
MIRROR LOAD	1.63u	1.22u	61.85u	6.25u	9.911	157.4m	209.7m	201.8m
TAIL CURRENT SOURCE	6.13u	590n	125.3u	12.5u	10.02	160m	195.6m	199.5m
2 nd stage input	4.8u	280n	630.7u	47.5u	13.28	114.8m	141m	150.6m

CL	5p
L1	890n
L2	1.22u
VICM	0.6
VIC...	0
L3	590n
VID	0
VIDAC	1
W1	8.22u
W2	1.63u
W3	6.13u
L4	280n
W4	4.8u

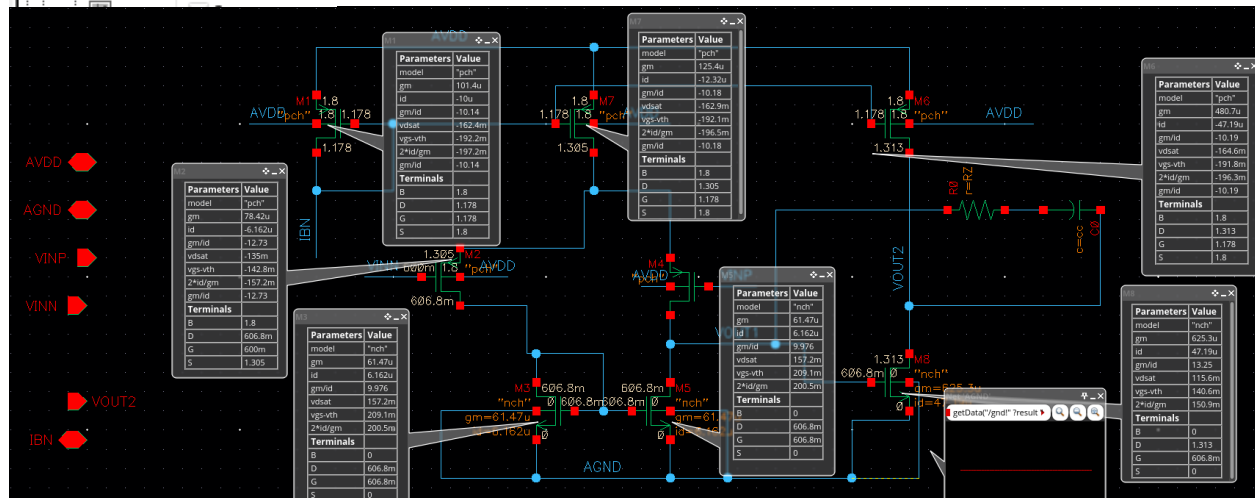


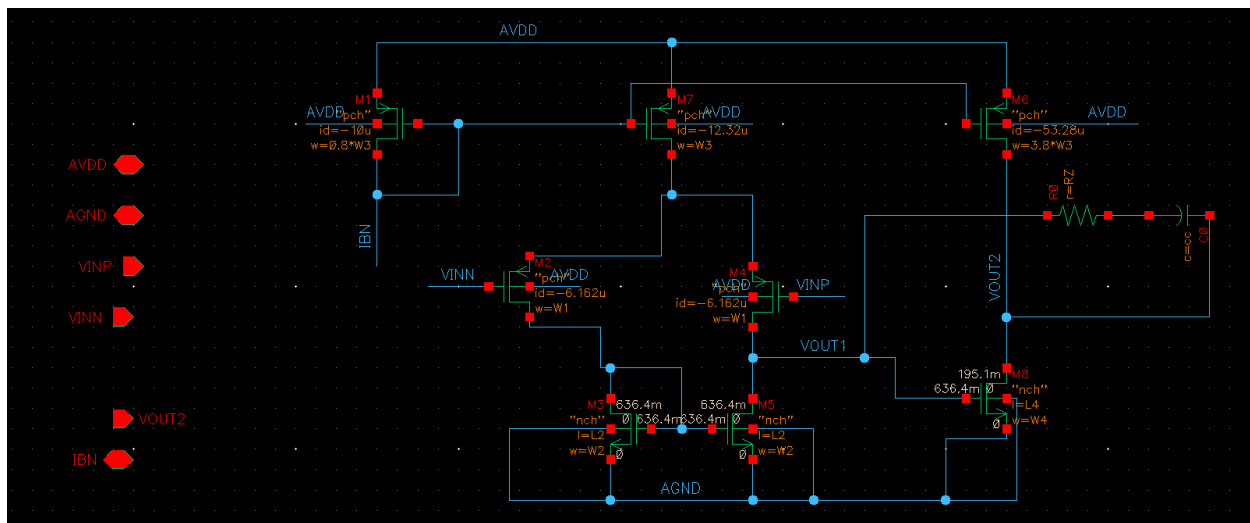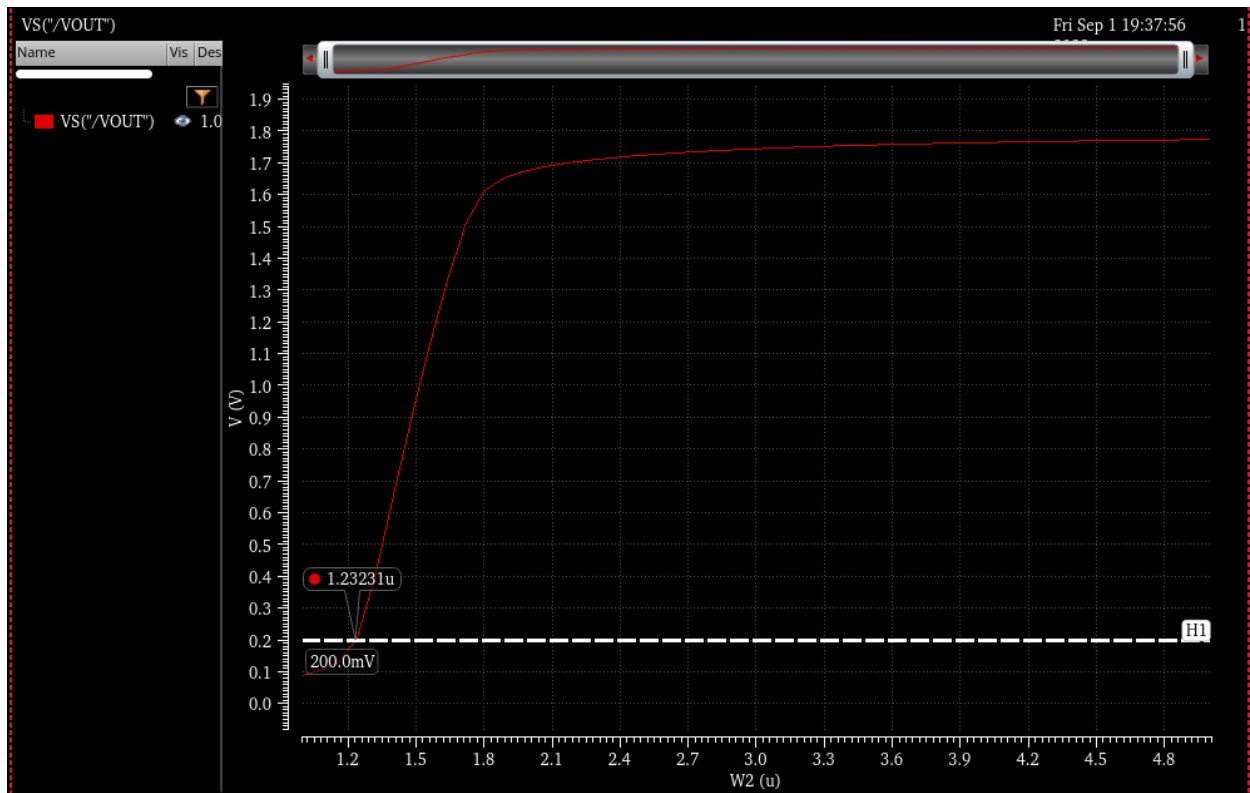THERE IS schematic offset made $v_{out}=1.313$, so we swept w (mirror load) to make $v_{out}=v_{dd}/2$.





So by doing cross multiplication (under same bias voltage there is a direct relation between width and current):
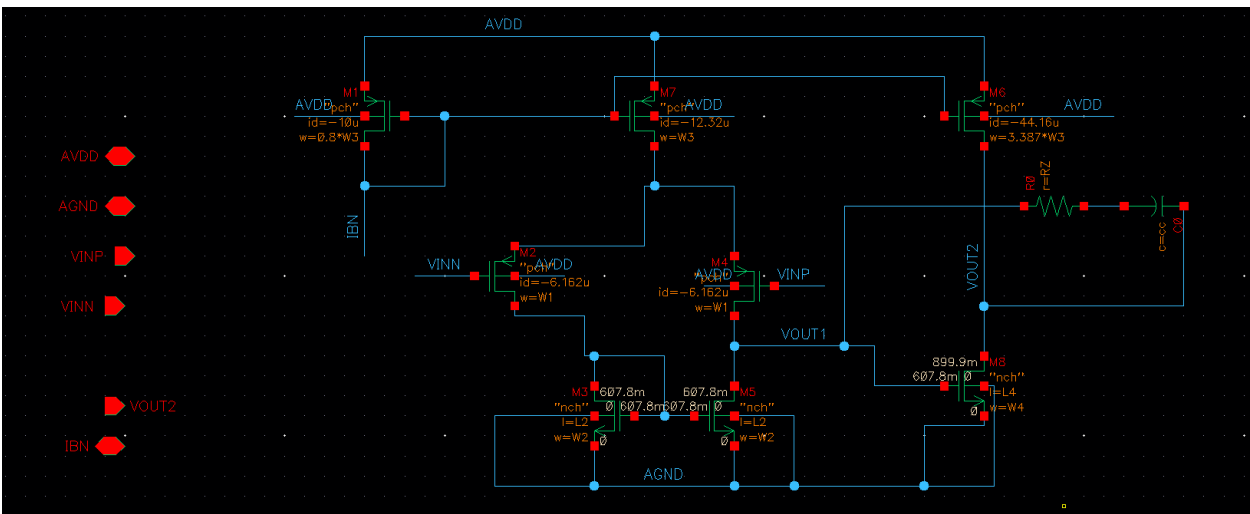
$$W6 = \frac{47.5 \cdot 3.8W3}{53.28} = 3.387W3$$



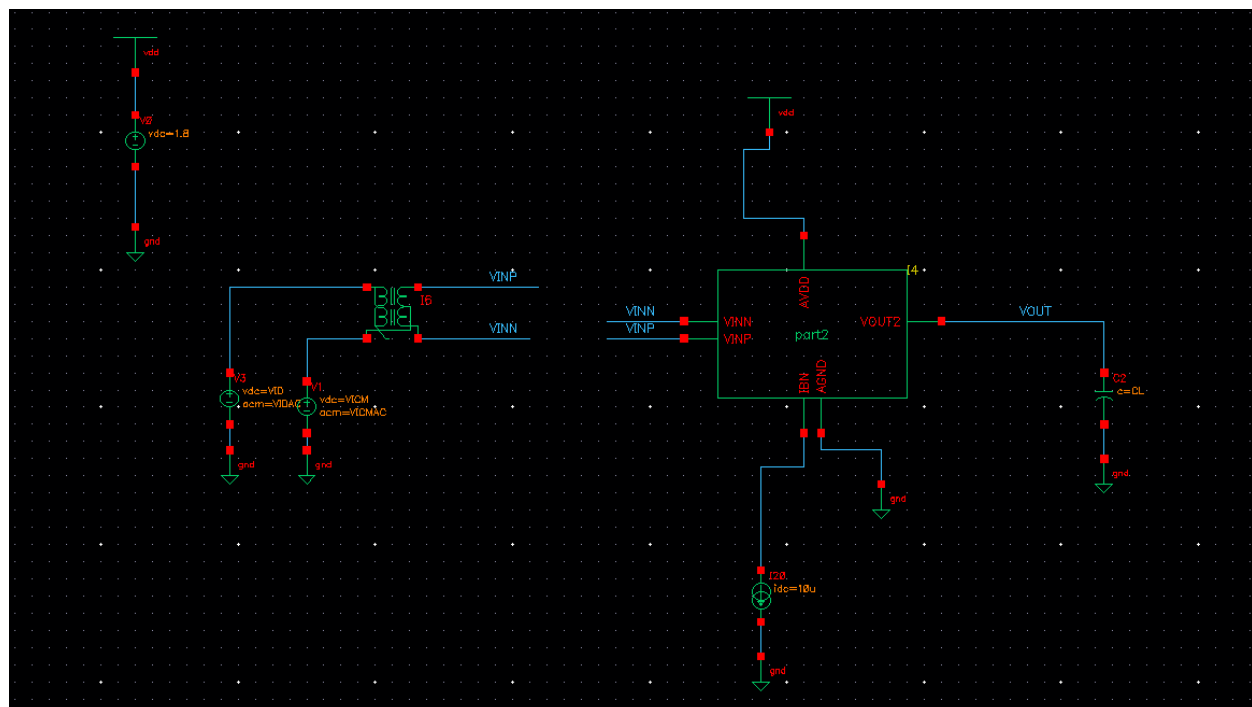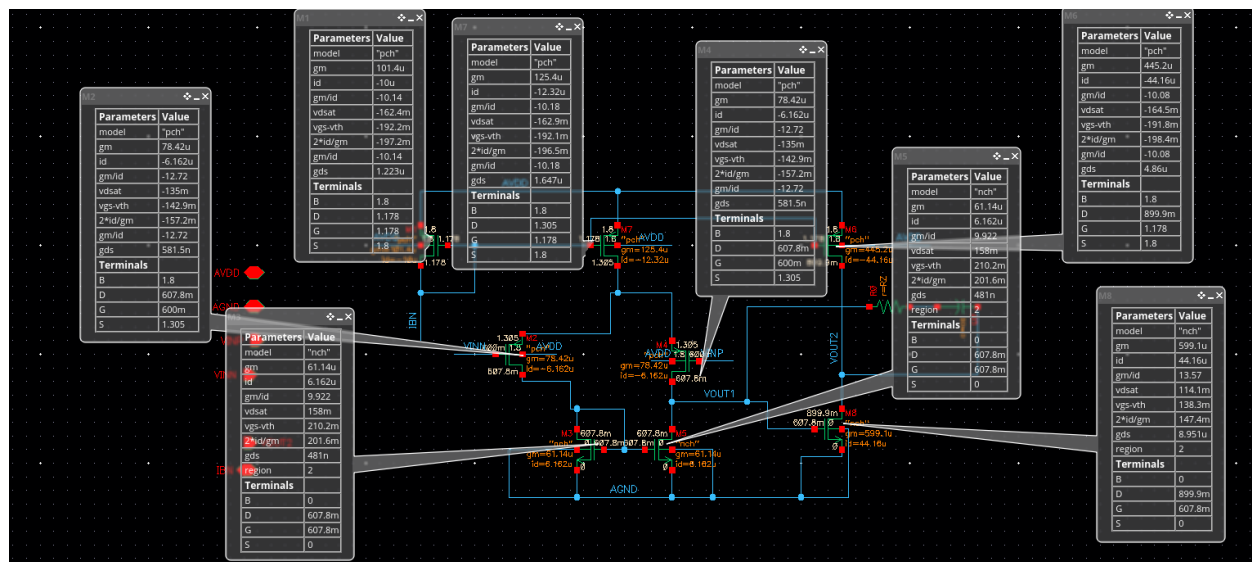1 SCHEMATIC OF THE OTA AND BIAS CIRCUIT WITH DC NODE VOLTAGES CLEARLY ANNOTATED.



1.1 IS THE CURRENT (AND GM) IN THE INPUT PAIR EXACTLY EQUAL?
YES, id=6.162u gm=78.42u

1.2 WHAT IS DC VOLTAGE AT THE OUTPUT OF THE FIRST STAGE? WHY?

613.3 mv, as $V_{OUT}=V_{GS}(M3)$ and M5 follow M3 and it is diode connected so $V_{GS}(0)=V_{GS}(1)=V_{DS}=607.8 \text{ mV}$

1.3 WHAT IS DC VOLTAGE AT THE OUTPUT OF THE SECOND STAGE? WHY?

$V_{DD}/2=0.9$, as $v_{gs}(m5)=v_{gs}(M8)$ so there is no schematic offset between the two transistors and as we know $v_{err} = \frac{\Delta V_{out}}{AV}$ so $\Delta V_{out} = 0$

2 DIFF SMALL SIGNAL CCS:

2.1 USE AC ANALYSIS (1Hz:10Gz, LOGARITHMIC, 10 POINTS/DECADE).

Choosing Analyses -- ADE Explorer

Analysis: ☐ tran ☐ dc ☒ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ acmatch
☐ stb ☐ pz ☐ lf ☐ sp
☐ envlp ☐ pss ☐ pac ☐ pstb
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp
☐ hb ☐ hbac ☐ hbstb ☐ hbnoise
☐ hbasp ☐ hbxf

AC Analysis

Sweep Variable
☒ Frequency
☐ Design Variable
☐ Temperature
☐ Component Parameter
☐ Model Parameter
☐ None

Sweep Range
☒ Start-Stop Start: 1 Stop: 10G
☐ Center-Span

Sweep Type
Logarithmic ☒ Points Per Decade: 10
☐ Number of Steps

Add Specific Points ☐
Add Points By File ☐

Specialized Analyses
None


Enabled ☒ Options...

OK Cancel Defaults Apply Help

2.2 CALCULATE CIRCUIT PARAMETERS (A_o, A_o IN dB, BW, GBW, UGF)

lab8_part3_1	A _o	3.189K			
lab8_part3_1	A _o _db	70.07			
lab8_part3_1	BW	1.507K			
lab8_part3_1	f _u	4.718M			
lab8_part3_1	GBW	4.805M			

2.3 PLOT DIFF GAIN (IN dB) VS FREQUENCY

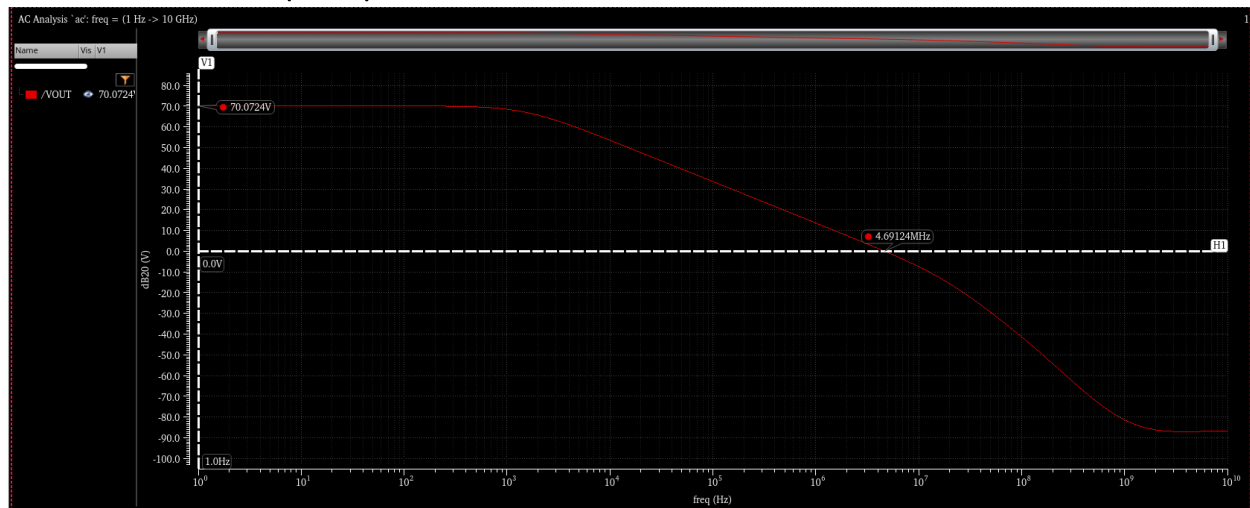

2.4 COMPARE SIMULATION RESULTS WITH HAND CALCULATIONS IN A TABLE.

$$A_{Vd} = g_{m_{I/P}} \left[\frac{1}{g_{ds_{I/P}} + g_{ds_{mirror}}} \right]$$

$$= 73,8 = \boxed{37,36} \text{ dB}$$

$$A_{Vd} = g_{m_{C8}} \left[\frac{2}{g_{ds8} + g_{ds6}} \right]$$

$$= 43,38 = 32,74 \text{ dB}$$

$$A_{Vd} = A_{Vd1} + A_{Vd2} = \boxed{70,10} \text{ dB}$$

$$= 3200 \text{ K}$$

$$B_{W1} = \frac{1}{2\pi R_{out1} (G_{M2} R_{out2}) C_c}$$


$$= 1559,26 \text{ Hz}$$

Handwritten calculation on lined paper:

$$GBW = UGF = A_{vB} \times BW = 3200 \times 1559 = 5.104M$$

	Simulated	Analytical
A0	3189	3200
A0_DB	70.07 db	70.10 db
BW	1507	1559
GBW	4.805M	5.104 M
Fu	4.718M	5.104 M


3 CM SMALL SIGNAL CCS:

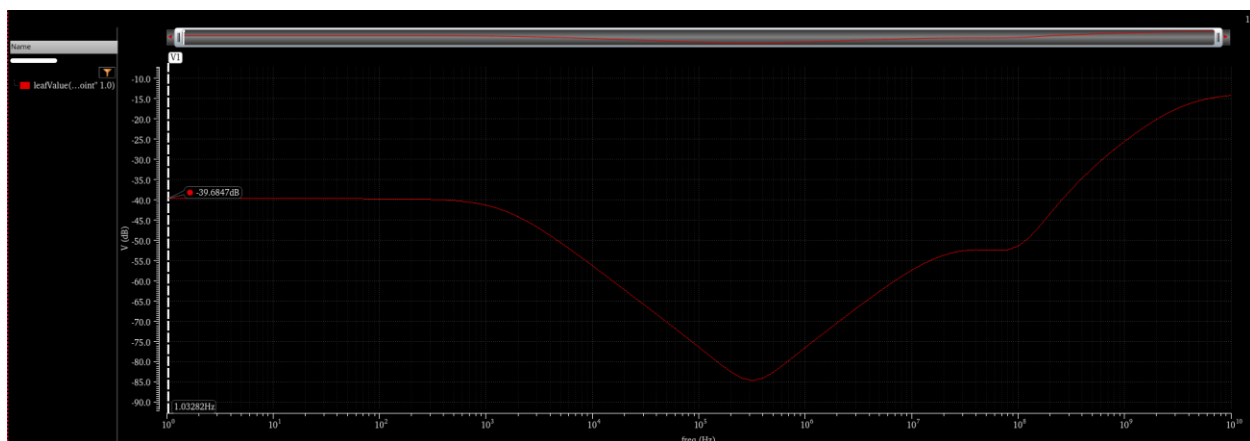

$$AV_{cm} = \frac{1}{2g_{m_{mirror}} * R_{SS}} = \frac{1}{2 * \frac{g_{m_{mirror}}}{g_{ds_{Tail}}}} = 0.0134 = -37.41db$$

	SIMULATOR	ANALYTICAL
AVcm	-39.68 db	-37.41 db

4 CM LARGE SIGNAL CCS (REGION VS VICM):


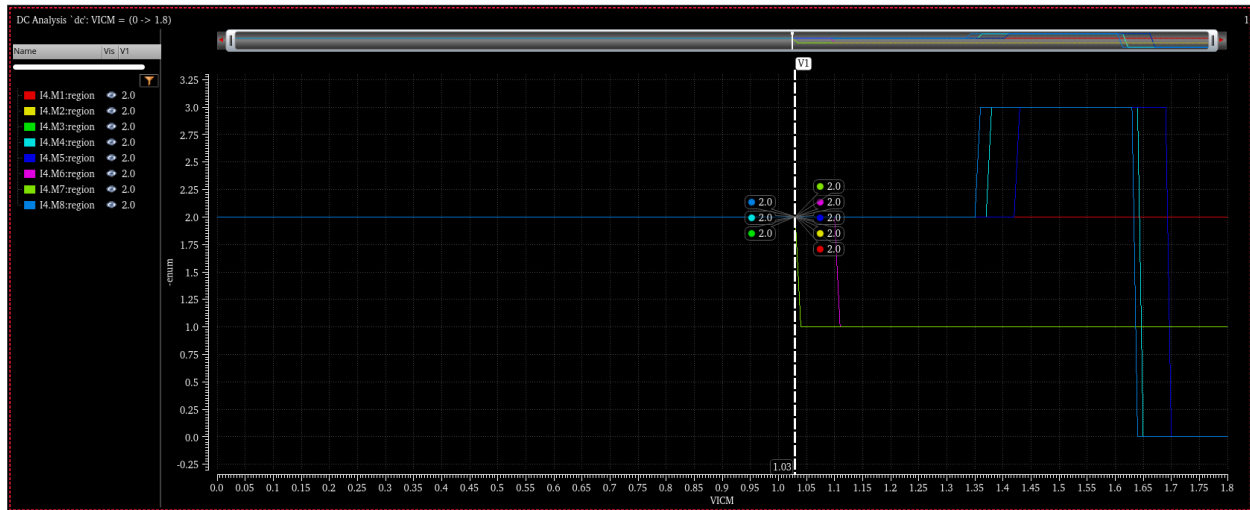



We uses PMOS input pair, body effect caused CMIR to extend till GND.

	Sim	Hand analysis
CMIR	$1.03 - 0 = 1.03$	$1 - 0.2 = 0.8$

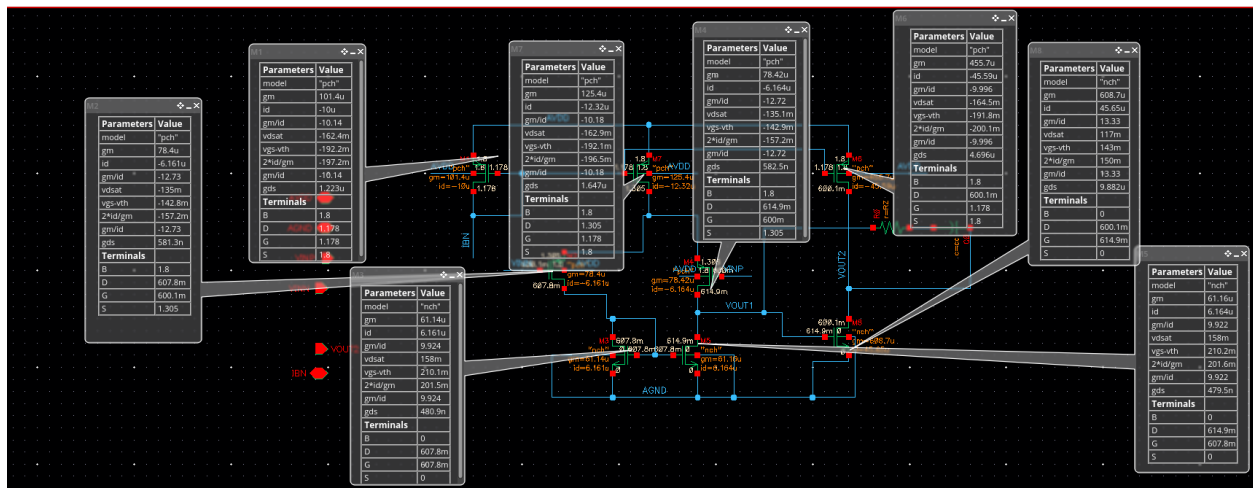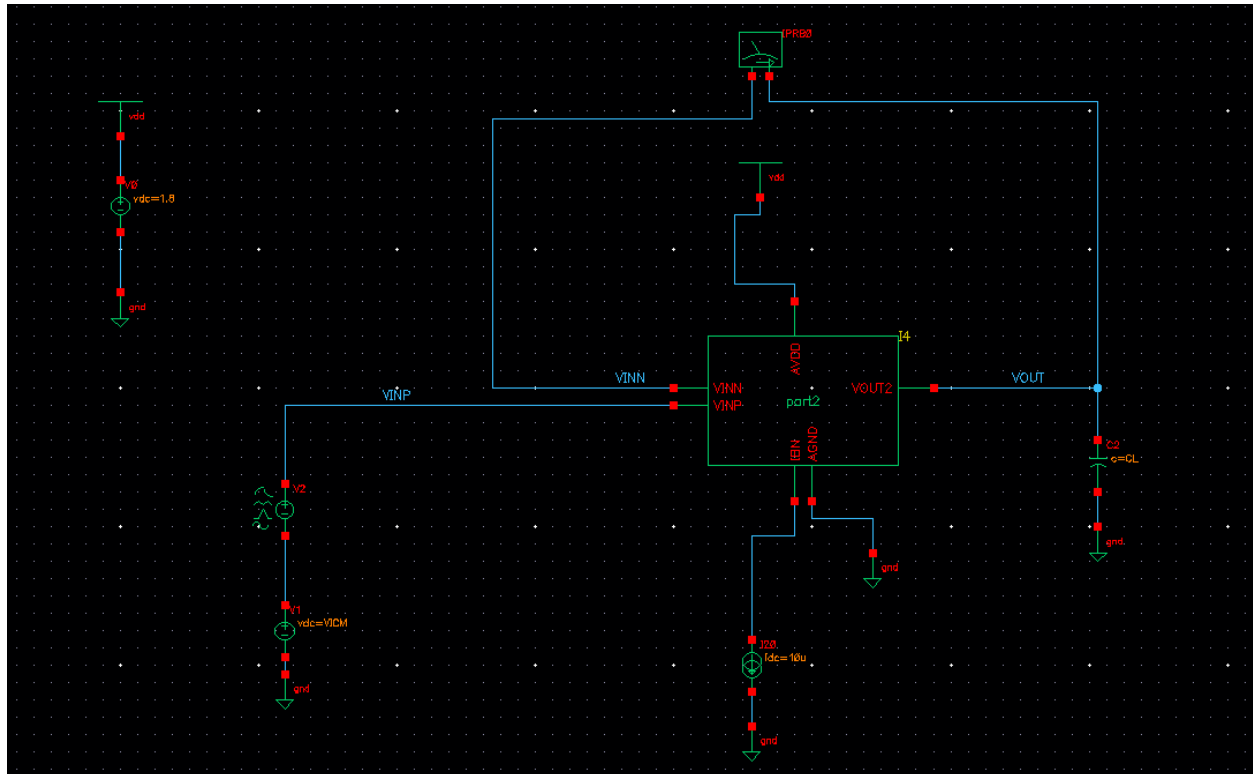PART 4: Closed-Loop OTA Simulation

1 SCHEMATIC OF THE OTA AND THE BIAS CIRCUIT WITH DC OP POINT CLEARLY ANNOTATED IN UNITY GAIN BUFFER CONFIGURATION.



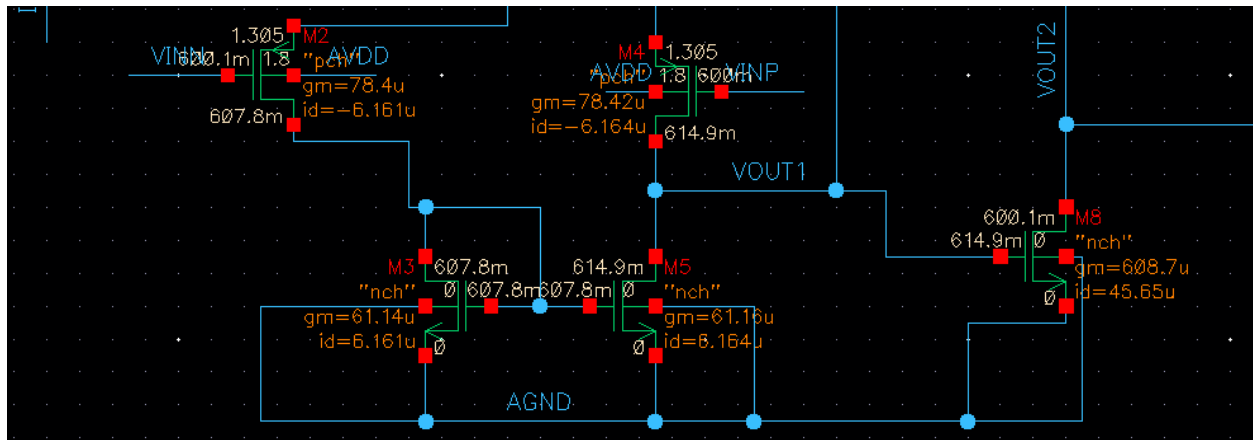

1.1 ARE THE DC VOLTAGES AT THE INPUT TERMINALS OF THE OP-AMP EXACTLY EQUAL? WHY?

NO, AS $\frac{\Delta V}{A_{ol}} = \frac{0.9-0.6}{3189} = 0.094mv \sim 1mv$

1.2 IS THE DC VOLTAGE AT THE OUTPUT OF THE FIRST STAGE EXACTLY EQUAL TO THE VALUE IN THE OPEN-LOOP SIMULATION? WHY?


NO, as we made unity buffer feedback, so $v_{out}=v_{in}=0.6v$ not $0.9v$.

1.3 IS THE CURRENT (AND GM) IN THE INPUT PAIR EXACTLY EQUAL? WHY?

No as there is a mismatch between the two inputs, as the output voltage deviates from its CM level and the gain is finite.

2 LOOP GAIN:

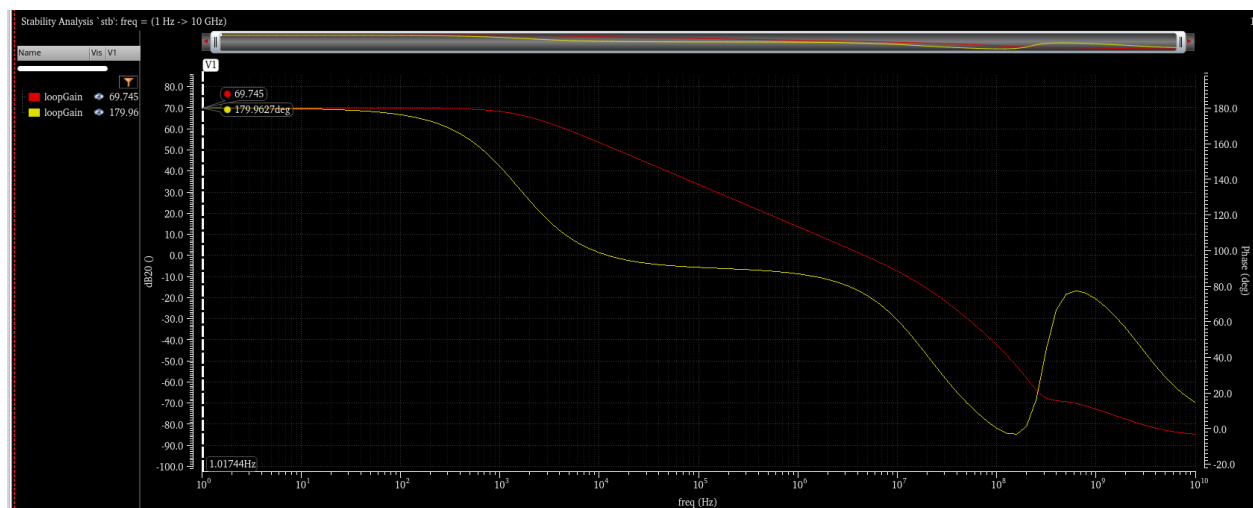2.1 PLOT LOOP GAIN IN dB AND PHASE VS FREQUENCY



2.2 COMPARE DC GAIN, FU, AND GBW WITH THOSE OBTAINED FROM OPEN-LOOP SIMULATION.


COMMENT

lab8_part4_1	A	3.071K			
lab8_part4_1	A_DB	69.75			
lab8_part4_1	BW	1.562K			
lab8_part4_1	FU	4.715M			
lab8_part4_1	GBW	4.795M			

	Open loop	Loop gain
A0	3189	3071
A0_DB	70.07 db	69.75 db
BW	1507	1562
GBW	4.805M	4.795 M
Fu	4.718M	4.715 M

The values are too close as expected, as $\beta=1$

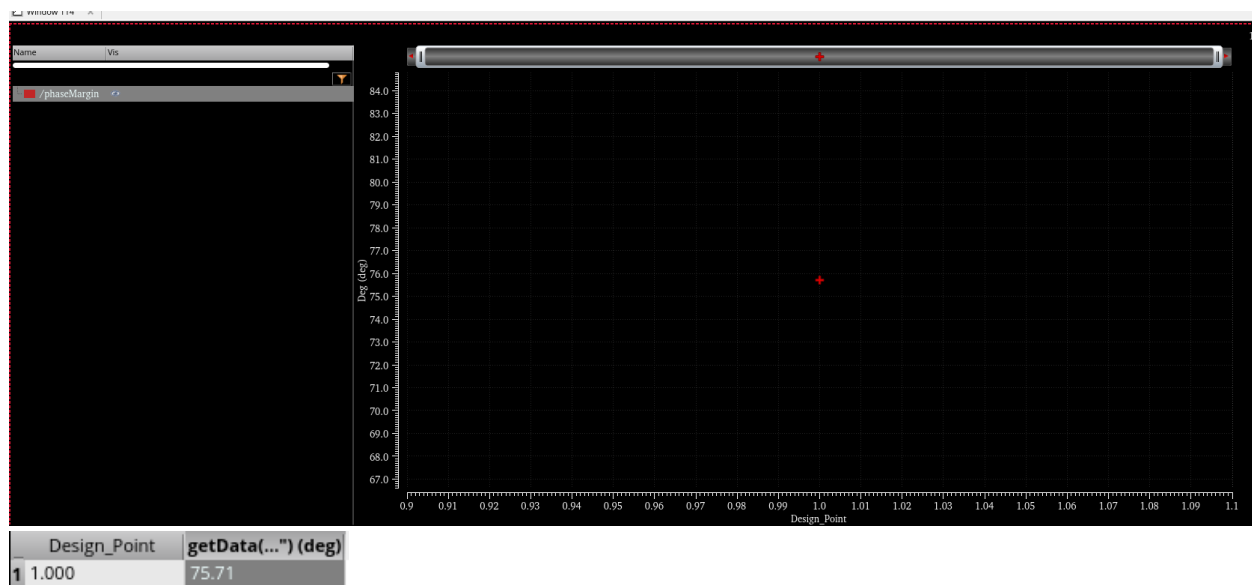2.3 REPORT PM. COMPARE WITH HAND CALCULATIONS. COMMENT.



Phase margin is too close to the analytical calculation, we made gm of the 2nd stage input is 8 times the gm of input stage and we expected a critical response (PM=76) but some variations happened made the pm a little less.

2.4 COMPARE SIMULATION RESULTS WITH HAND CALCULATIONS IN A TABLE.

	Loop gain	Analytical
A0	3071	3200
A0_DB	69.75 db	70.10 db
BW	1562	1559
GBW	4.795 M	5.104 M
Fu	4.715 M	5.104 M

For analytical calculations $\text{loopgain} = \beta A_{ol}$, and $\beta = 1$ so $\text{loopgain} = A_{ol}$ that we calculated above.

3 SLEW RATE:


- 3.1 APPLY A STEP INPUT WITH THE FOLLOWING PARAMETERS (DELAY = 1US, INITIAL VALUE = CMIR-LOW + 50mV, FINAL VALUE = CMIR-HIGH – 50mV, RISE TIME = 1nS, PERIOD = 1s, WIDTH = 1s). NOTE THAT WE WANT A SINGLE STEP INPUT, WHICH IS WHY WE SELECTED VERY LARGE PERIOD AND WIDTH FOR THE PULSE.

The screenshot shows the 'Edit Object Properties' dialog box for a pulse source. The dialog is organized into several sections:

- Cell Name:** vsource
- View Name:** symbol
- Instance Name:** V2
- User Property:** Master Value, Local Value, Display
- lvIgnore:** TRUE
- CDF Parameter:** A table with columns for the parameter name, its value, and a display toggle.
- Display small signal params:** unchecked
- Display temperature params:** unchecked
- Display noise parameters:** unchecked

CDF Parameter	Value	Display
DC voltage		off
Source type	pulse	off
Frequency name 1		off
Delay time	1u s	off
Zero value	250m V	off
One value	950m V	off
Period of waveform	1 s	off
Rise time	1n s	off
Fall time		off
Type of rising & falling edge		off
Pulse width	1 s	off

3.2 REPORT VIN AND VOUT OVERLAID

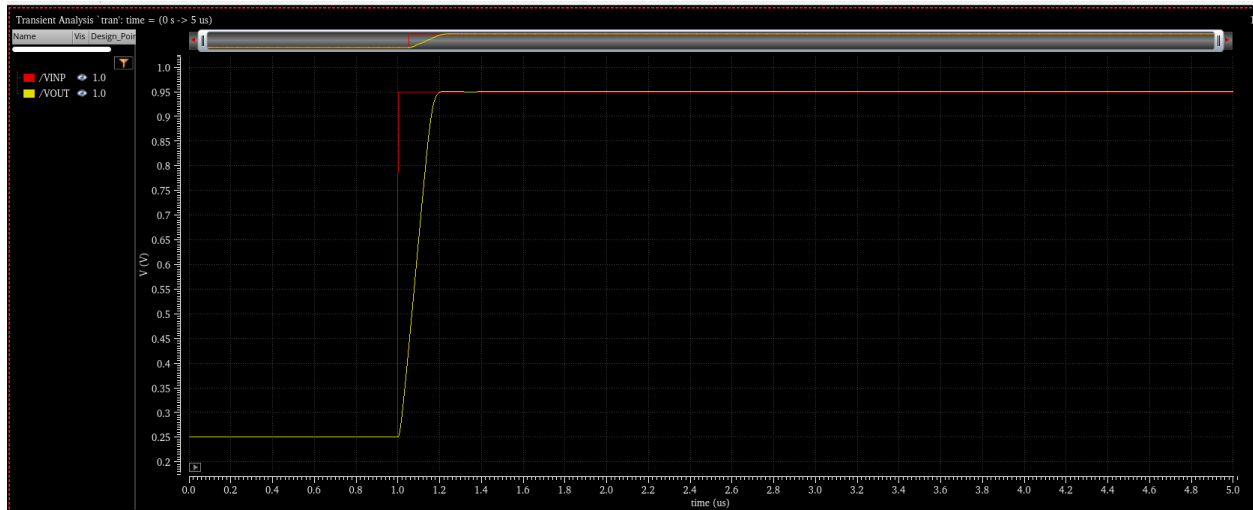

3.3 REPORT THE SLEW RATE.


Test	Output	Nominal	Spec	Weight	Pass/Fail
Filter	Filter	Filter	Filter	Filter	Filter
lab8_part4_1	slewRate(VT("/VOUT") 0.25 nil 0.95 nil 10 90 nil "time")	4.409M			

3.4 COMPARE SIMULATION RESULTS WITH HAND CALCULATIONS IN A TABLE

It Is less than the expected value 5 but we can decrease cc to get slew rate >5
But we should make sure the new value of cc doesn't violate the PM specs which is happened successfully.

Simulator spectre					
Analyses					
stb 1 10G 10 /IPRB0 Lo...					
tran 0 5u conservative					
dc t					
ck to add analysis					
Design Variables					
cc 2.15p					

Test	Output	Nominal	Spec	Weight	Pass/Fail
Filter	Filter	Filter	Filter	Filter	Filter
lab8_part4_1	slewRate(VT("/V...)	5.07M			

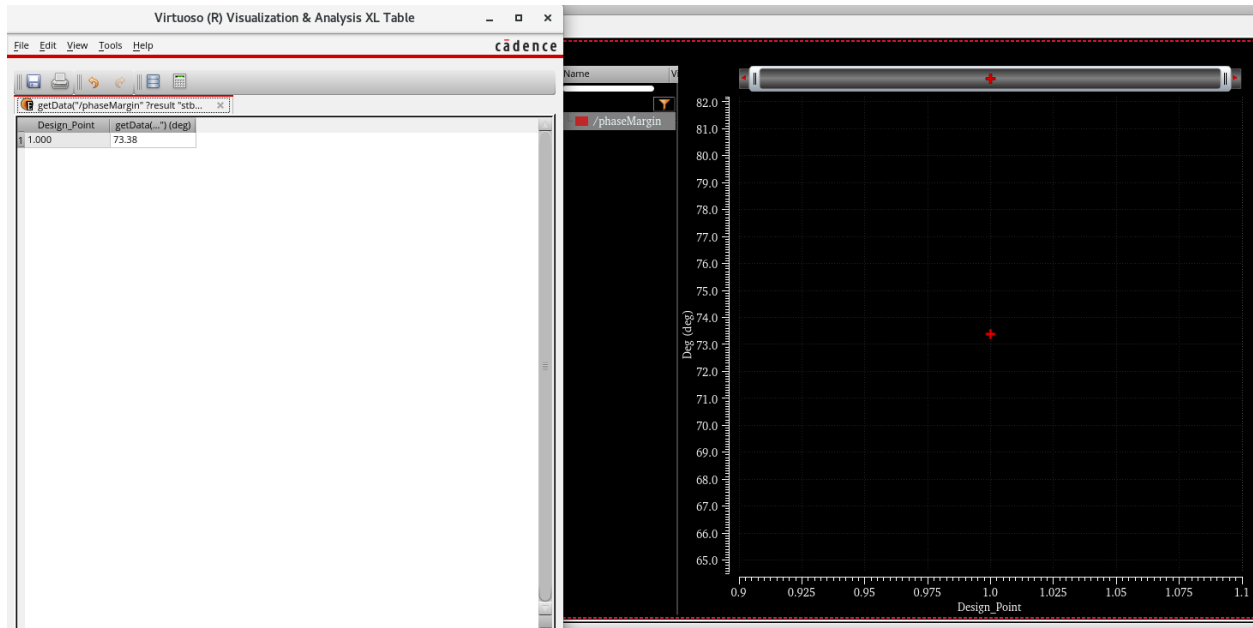

Cc	Sim	Analytical
2.5p	4.41	$(12.5/2.5) = 5$
2.15p	5.07	$(12.5/2.15) = 5.814$

- 4 APPLY A SMALL SIGNAL STEP INPUT WITH THE FOLLOWING PARAMETERS (DELAY = 1US, INITIAL VALUE = THE MIDDLE OF THE CMIR, FINAL VALUE = THE MIDDLE OF THE CMIR + 5mV, RISE TIME = 1NS, PERIOD = 1s, WIDTH = 1s). NOTE THAT WE WANT A SINGLE STEP INPUT, WHICH IS WHY WE SELECTED VERY LARGE PERIOD AND WIDTH FOR THE PULSE. NOTE THAT WE APPLY A SMALL SIGNAL PULSE (5mV STEP) TO MEASURE THE SMALL SIGNAL SETTLING TIME.


The screenshot shows the 'Edit Object Properties' dialog box for a pulse source. The 'View Name' is 'symbol1' and the 'Instance Name' is 'V2'. The 'User Property' section shows 'IvsIgnore' set to 'TRUE'. The 'CDF Parameter' section lists various parameters for a pulse source, including 'DC voltage', 'Source type' (set to 'pulse'), 'Frequency name 1', 'Delay time' (1u s), 'Zero value' (600m V), 'One value' (605m V), 'Period of waveform' (1 s), 'Rise time' (1n s), 'Fall time', 'Type of rising & falling edge', 'Pulse width' (1 s), 'Display small signal params', 'Display temperature params', 'Display noise parameters', and 'Multiplier'. Each parameter has a corresponding 'Value' field and a 'Display' toggle set to 'off'.

CDF Parameter	Value	Display
DC voltage		off
Source type	pulse	off
Frequency name 1		off
Delay time	1u s	off
Zero value	600m V	off
One value	605m V	off
Period of waveform	1 s	off
Rise time	1n s	off
Fall time		off
Type of rising & falling edge		off
Pulse width	1 s	off
Display small signal params	<input type="checkbox"/>	off
Display temperature params	<input type="checkbox"/>	off
Display noise parameters	<input type="checkbox"/>	off
Multiplier		off

4.1 CALCULATE THE OUTPUT RISE TIME FROM SIMULATION.

```
riseTime(mag(leafValue( v("/VOUT" ?result "tran") "Design_Point" 1 )) 600m nil 605m nil 10 90 nil "time")
```

	Expression	Value
1	riseTime(mag(le...	50.10E-9

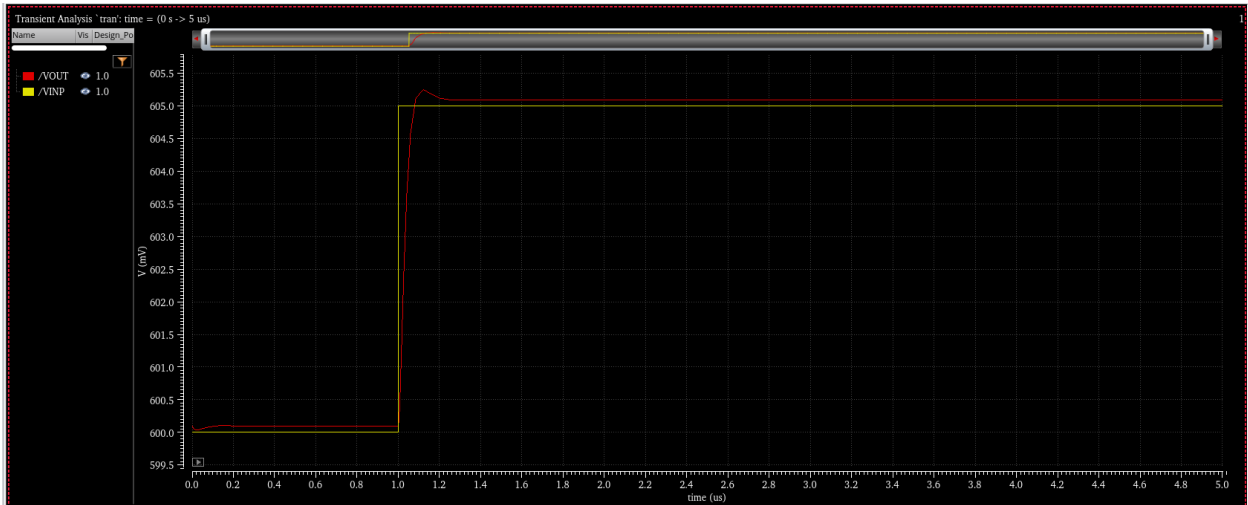


4.2 COMPARE SIMULATION RESULTS WITH HAND CALCULATIONS IN A TABLE

HAND CALCULATION	Simulation
$\frac{2.2}{2\pi * UGF(in\ hz)} = \frac{2.2}{2\pi * 5.104 * 10^6} = 68.6n$	50.1n

As written in the hint, using $t_{rise} = 2.2\tau$ is based on first-order model, and first-order model is an approximation to the overdamping system which is too slow, but as we showed above the phase margin is 75.7 which is second order under damping system which is too close to critical damping.

4.3 DO YOU SEE ANY RINGING? WHY?

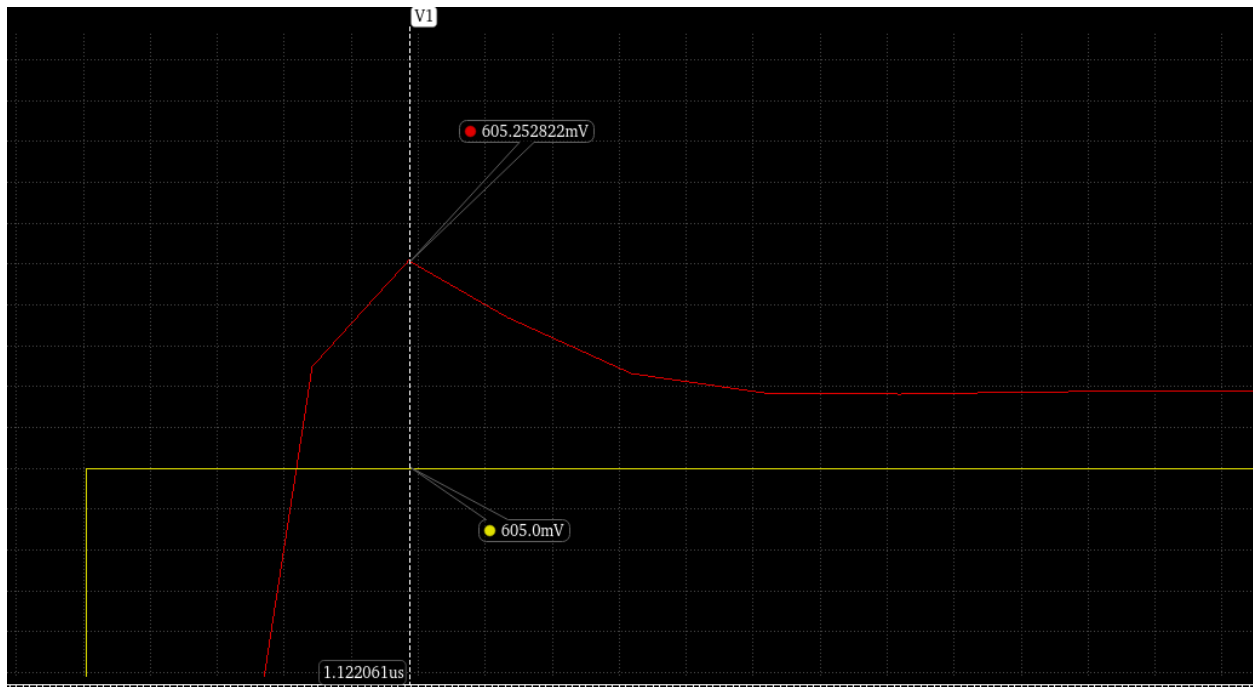


yes, there is an over shoot as the phase margin is 75.7 which is second order underdamped system, and if we increased the PM to be more 76 (critical) we wouldn't see any, and there is also no oscillations as PM is not too small.

If we used the new cc=2.15p :

lab8_part4_1	A0	3.071K			
lab8_part4_1	A0_DB	69.75			
lab8_part4_1	BW	1.819K			
lab8_part4_1	FU	5.432M			
lab8_part4_1	GBW	5.585M			
lab8_part4_1	/phaseMargin_stb_margin	73.6			

lab8_part4_1	slewRate(VT("/V...	5.07M			
--------------	--------------------	-------	--	--	--

Expression	Value
1 riseTime(leafVal...	43.62E-9

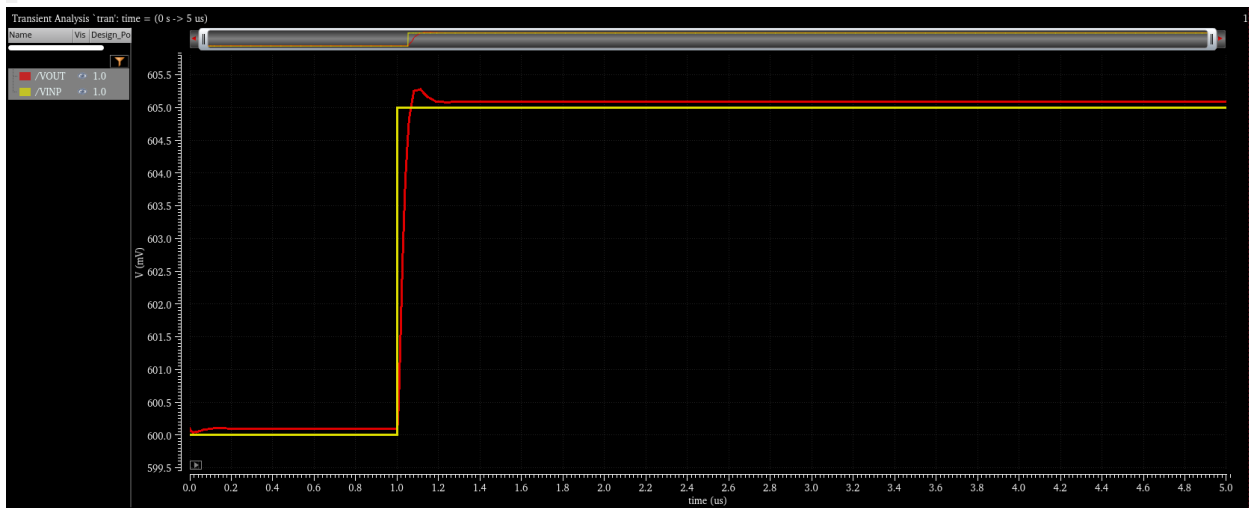

$$[\text{Trise (analytical)}] = \frac{2.2}{2\pi * UGF(in \text{ hz})} = \frac{2.2}{2\pi * 5.432 * 10^6} = 64.46 \text{ ns}$$

ALL THE SPECS ARE NOT VIOLATED